

Q.1 14.1 of Razavi's

Q.2 14.2 of Razavi's



Q.3 14.3 of Razavi's

Q.4 14.13 of Razavi's

Q.5 15.2 of Razavi's

Q.6

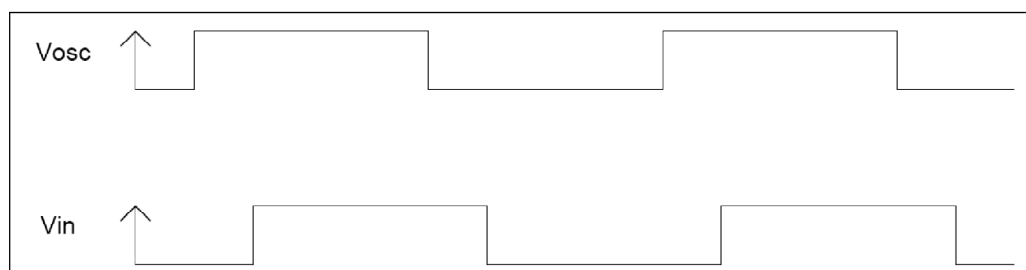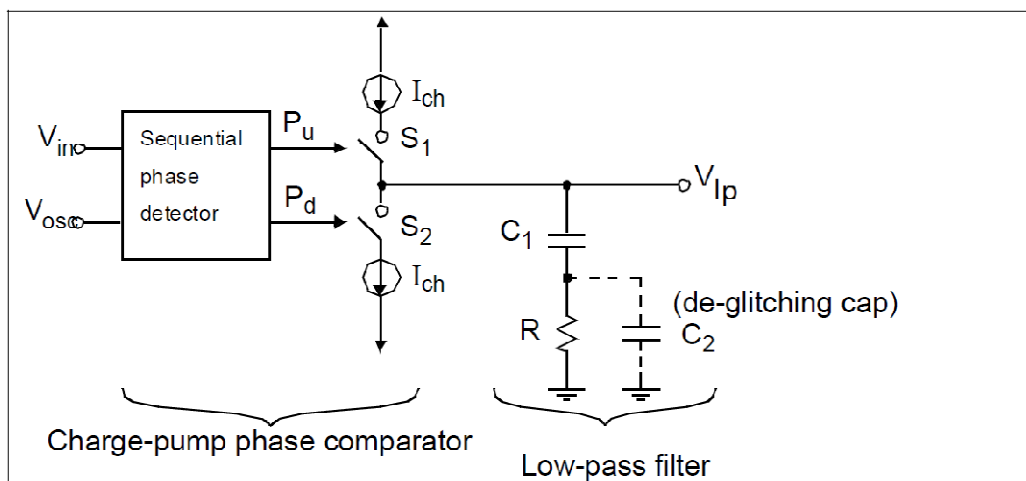a) A charge-pump phase comparator for integrated PLLs is shown below. There is also an example of two waveforms related to it, V_{osc} and V_{in} . Draw the related P_u and P_d waveforms and explain briefly how they relate to V_{in} and V_{osc} .



b) CMOS technology still continues toward finer scale geometries. Do you think that this development could make any influence on the choice of PLL architectures? Could you explain why and how?