

# Nyquist Digital to Analog Converters

Tuesday, February 22nd, 9:15 – 11:10

Snorre Aunet (sa@ifi.uio.no)  
Nanoelectronics group  
Department of Informatics  
University of Oslo



## February the 15th

- 1.1 The ideal data converter
- 1.2 Sampling
  - 1.2.1 Undersampling
  - 1.2.2 Sampling-time jitter
- 1.3 Amplitude Quantization
  - 1.3.1 Quantization noise
  - 1.3.2 Properties of the Quantization Noise
- 1.4 kT/C Noise
- 1.5 Discrete and Fast Fourier Transform
  - 1.5.1 Windowing
- 1.6 Coding Schemes
- 1.7 The D/A Converter
  - 1.7.1 Ideal reconstruction
  - 1.7.2 Real Reconstruction
- 1.8 The Z-transform
- (The contents refer to "Maloberti")



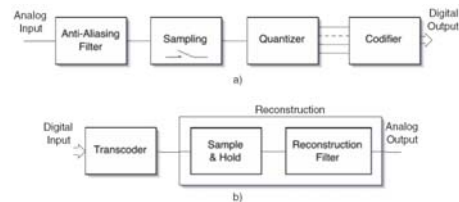


Figure 1.1. Block diagram of the basic functions of an A/D (a) and a D/A (b) converter.

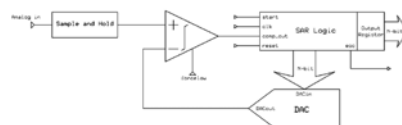

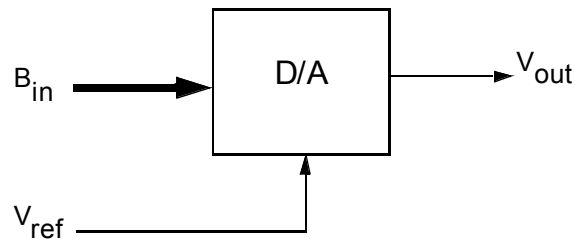

## Ideal D/A converter



$$B_{in} = b_1 2^{-1} + b_2 2^{-2} + \dots + b_N 2^{-N}$$

$$V_{out} = V_{ref}(b_1 2^{-1} + b_2 2^{-2} + \dots + b_N 2^{-N})$$

## February the 22th



- **3.1 Introduction**
- 3.1.1 DAC applications
- 3.1.2 Voltage and current references
- **3.2 Types of converters**
- **3.3 Resistor based architectures**
- 3.3.1 Resistive divider
- 3.3.2 X-Y selection
- 3.3.3 Settling of the output voltage
- 3.3.4 Segmented architectures
- 3.3.5 Effects of mismatch
- 3.3.6 Trimming and calibration
- 3.3.7 Digital Potentiometer
- 3.3.8 R-2R Resistor Ladder DAC
- 3.3.9 Deglitching

- **3.4 Capacitor based architectures**
- 3.4.1 Capacitive divider DAC
- 3.4.2 Capacitive MDAC
- 3.4.3 "Flip around" MDAC
- 3.4.4 Hybrid capacitive resistive DACs

- **3.5 Current source based architectures**
- 3.5.1 Basic operation
- 3.5.2 Unity current generator
- 3.5.3 Random mismatch with unary selection
- 3.5.4. Current sources selection
- 3.5.5 Current switching and segmentation
- 3.5.6 Switching of current sources
- **3.6 Other architectures**  
(The contents refer to "Maloberti")



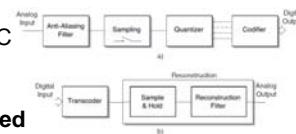


Figure 1.1. Block diagram of the basic functions of an AD (a) and a DA (b) converter.

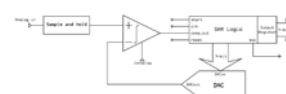

26. februar 2011 4

# Real reconstruction filters

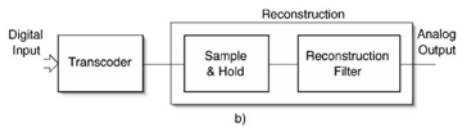

$$H_{S\&H}(s) = \frac{1 - e^{-sT}}{sT}, \quad (1.39)$$

where  $\tau$  is a suitable gain factor whose dimension is time for making  $H_{S\&H}$  dimensionless.

Equation (1.39) on the  $j\omega$  axis becomes

$$H_{S\&H}(j\omega) = j \frac{T}{\tau} e^{-j\omega T/2} \frac{\sin(\omega T/2)}{\omega T/2}, \quad (1.40)$$

showing a phase shift proportional to  $\omega$  and an amplitude attenuation proportional to the *sinc* ( $=\sin(x)/x$ ) function.

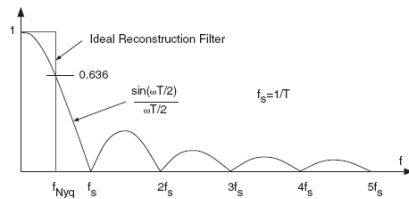


Figure 1.27. Amplitude response of the ideal and real sample-and-hold.

- A real reconstruction filter is an approximation of the ideal reconstruction response, given by eq. 1.39.
- Many commercial DACs provide output in sampled data form (no reconstruction)
- A reconstruction filter removes frequencies higher than the Nyquist limit. (Still harmonics of low frequency signals and the intermodulation products coming from multi-tone inputs produce spurs inside the first Nyquist zone.)
- Other DACs have an output providing a continuous time signal with a BW within the first Nyquist zone.
- For example, both the input and the output for audio equipment is sampled at 44.1 kHz. Both audio filters block as much as possible above 22 kHz and pass as much as possible below 20 kHz. Typically both filters are active op-amp filters, with exactly the same selection of resistors and capacitors.

# Matching of passive components (R, C) within 0.1 to 0.02 % possible

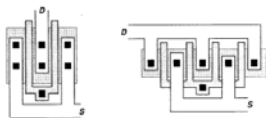


Figure 18.9 (a) Simple folding of a MOSFET, (b) use of multiple stages

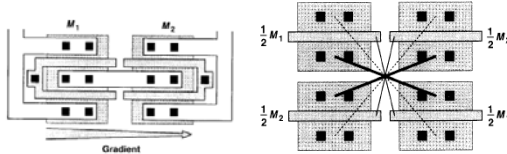


Figure 18.18 Effect of gradient in a differential pair.

Figure 18.19 Common-centroid layout.


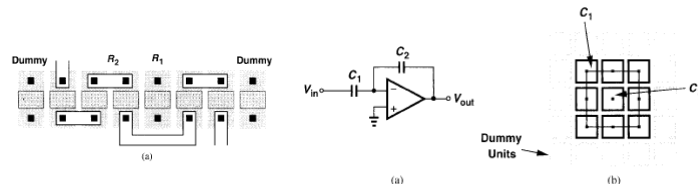


Figure 18.35


- Gain or attenuation of references
- Careful layout (inter digitized , common centroid, dummy elements, equalization of resistive metal contacts) leads to matching accuracies within 0.02 % to 0.1 % without trimming or digital correction (60 dB to 70 dB resolution)

# DACs, CMOS switches and OTAs

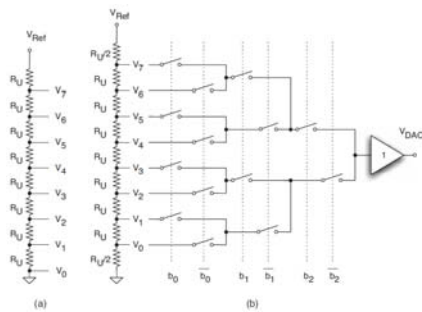

- A MOS transistor becomes an **off-switch** if its driving voltage is in the **subthreshold** region, and low resistance (**on-switch**) if its driving voltage well **exceeds the threshold** and  $V_{DS}$  is small.
- Design of switches and their control is an important part of the data converter design because it is important to obtain **low on-resistance**, **high speed of switching** and **minimum side effects** (clock feedthrough, charge injection).
- OTA performance crucial for meeting DAC specifications

## (A few) applications (ch. 3.1.1)

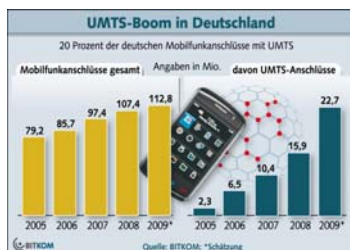

- High speed DACs for video signals from a computer or a DVD.
- HDTV: (plasma) requires above 11 bits. 12-bits and 150 MSPS often required
- UMTS, CDMA2000, GSM/EDGE; 200 MSPS 12 – 16 bit can be necessary.
- DACs may replace potentiometers in analogue signal processors.
- Audio; 16-bit (or more), 44 kSpS

# Voltage and current references (ch. 3.1.2)


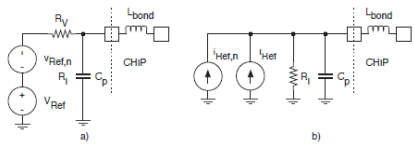


Figure 3.2. Equivalent model of external references: (a) voltage and (b) current.


**Remember**  
 The noise of reference generators must be lower than the expected quantization noise floor. The request becomes very challenging for resolutions above 14-bit.

- The dynamic range is established by the voltage (or current) reference which can be generated inside the chip or via an external pin.
- High accuracy is needed as errors affect the overall performance.
- **Constant**, independent of load changes, temperature, supply voltage, time
- Static errors may lead to gain errors.
- **Dynamic** errors are worse, and may affect **SNR** and speed.


# 3 main types of converters

 

 
- **Resistor** based architectures
- **Capacitor** based architectures
- **Current source** based architectures


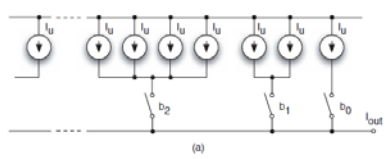
$$V_{Out} = V_{Ref} \frac{C_1}{C_1 + C_2} \quad (3.18)$$


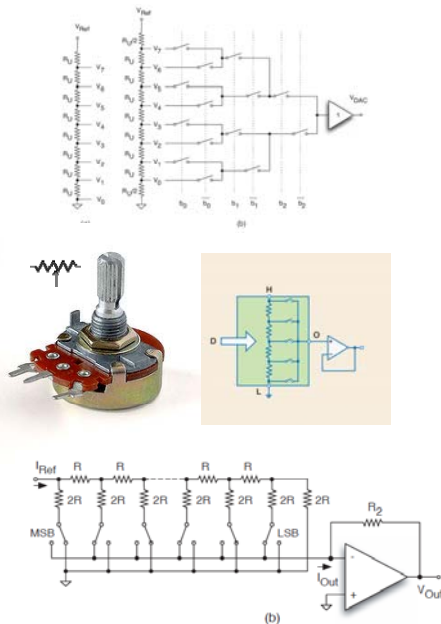
## Resistor based architectures (ch. 3.3)



- Resistive divider.
- The digital potentiometer
- R-2R resistive ladder
- $\Omega/\square$  -  $k\Omega/\square$
- Matching errors cause gain errors and sometimes harmonic distortion
- When ratio between resistors is an integer number, use unity elements to construct the various elements by series connections.
- Dummy structures for improved matching

$$R = \rho_{\square}(L/W)_{eff} + 2 \cdot R_{cont.}$$

## Resistor divider (ch. 3.3.1)

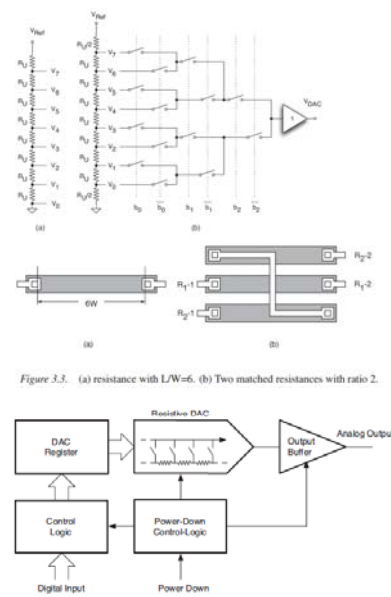


Figure 3.3. (a) resistance with  $L/W=6$ . (b) Two matched resistances with ratio 2.

- A resistive string connected across the positive and negative reference obtain multiple voltages whose digitally controlled selection realizes a very simple DAC.
- Fig. 3.4 a); 3-bit divider made of  $2^3$  equal resistors.
- The selected voltage (simple method shown in Fig. 3 b) )is used as the input of a buffer (high input impedance, low output impedance)
- Switch on resistances and the parasitic capacitances can impede the fast operation of a DAC.
- Fig. 3.5 : typical architecture. Power on reset for zero outputvoltage at power-on. Serial interface may be used for input data.

Figure 3.5. Typical architecture of a resistive divider DAC.

## X-Y Selection (ch. 3.3.2)

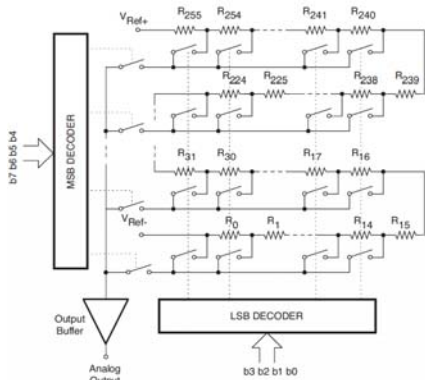


Figure 3.6. Resistive DAC with X-Y addressing scheme.

- Fig. 3.6: 256 unity resistances divided into 16 lines.
- Avoids the excessive growth of switches with number of bits as the resistive divider architecture (needing 510 switches and 256 logic signals driving the switches for an 8-bit DAC).
- Decoding signals are  $2 \cdot 2^{n/2}$  instead of  $2^n$ .
- (8 bit: 32 instead of 256.)
- The layout is compact and **minimizes the grading error**
- The time constant of the RC network between resistive divider and buffer is doubled (2 switches instead of one).

## Settling of the output voltage (ch. 3.3.3)

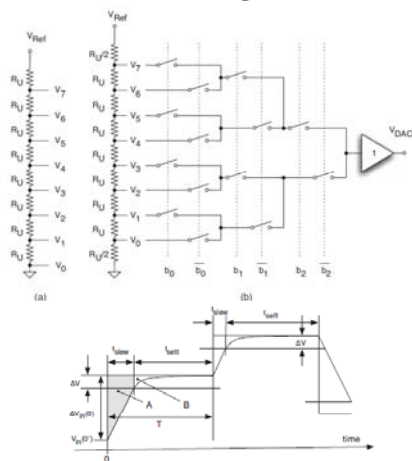


Figure 3.8. Response of a unity gain buffer with finite slew-rate and bandwidth.

### Observation

A code dependent settling of the output voltage causes distortion. High SFDR requires low resistances at every node. The variation of the settling time must be much smaller than the hold period.

- The RC network and the buffer determine the time from a change in input code to the step change on the output has settled.
- The response is fastest if the beginning or end of the resistive string are selected and slower in the middle range.
- A reconstruction filter filter out spurs at frequencies higher than the Nyquist limit.
- Harmonics of low frequency signals and intermodulation products produce spurs inside the first Nyquist zone. Thus, a spur free output spectrum requires a settling time well below the D/A conversion period ( $\rightarrow$  low unity resistance).
- The buffer must also be fast enough (limited by SR and gain bandwidth product).

## Segmented architectures (ch. 3.3.4)

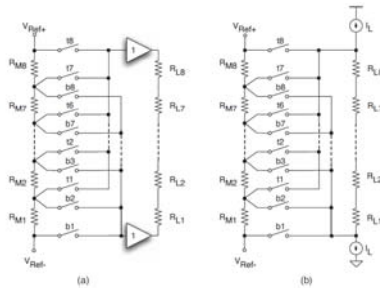


Figure 3.10. (a) Cascade of two DACs with decoupling buffers. (b) Volt-metric interconnection of the LSB DAC.

- Obtains a higher resolution by combining the operation of two or more DACs together.
- **Fig. 3.10 a):**  $R_{M1}$ - $R_{M8}$  obtain a 3 bit coarse division, and  $R_{L1}$  -  $R_{L8}$ ,  $i=1\dots 8$ .
- Switches select one of the coarse intervals.
- The offset of the buffers must match below one LSB.
- The input impedance of the input buffer needs to be high and the output resistance must be much less than the total resistance of the LSB divider.
- **Fig. 3.10 b):** Two current generators inject and drain the same current (setting the current in the connections between the two DACs to zero.)

## Effect of the mismatch (ch. 3.3.5)



$$R_i = R_u(1 + \epsilon_a) \cdot (1 + \epsilon_{r,i}), \quad (3.9)$$

The  $k$ -th resistor is

$$R_k = R_0(1 + k \cdot \alpha \Delta X); \quad k = 0, \dots, 2^n - 1 \quad (3.12)$$

and the output at the tap  $k$  becomes

$$V_{out}(k) = V_{ref} \frac{k + \alpha \Delta X \cdot k(k+1)/2}{2^n - 1 + \alpha \Delta X \cdot (2^n - 1)2^n/2} \quad (3.13)$$

which is parabolic with initial value 0 and final value  $V_{ref}$ . Recall that the INL is  $V_{out}(k) - V_{ideal}(k)$ . It is plotted in Fig. 3.11 for an 8-bit DAC with  $\alpha \Delta X = \pm 10^{-4}$  (curves (a) and (b)). Notice that the maximum value of the INL



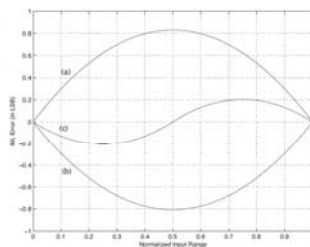


Figure 3.11. INL caused by a gradient in the specific resistance for a linear and a folded (curve (c)) resistive string.

- Global error and local fluctuations of parameters
- The error depends on accumulation of mismatches and is zero at the two ends of the string.
- Problematic when errors are correlated and accumulate to a large INL.
- Fig.3.11: 8-bit DAC with  $\alpha \Delta X = \pm 10^{-4}$
- ( $\Delta X$  is the spacing between unity elements.) (curves a) and b)) Max INL  $\pm 0.8$  LSB.
- Fig. 3.11 c) has a resistive divider folded around it's midpoint, where the INL becomes zero. The max INL is reduced to  $1/4$ .
- Better results are obtained with multiple folding and suitably designed layouts.

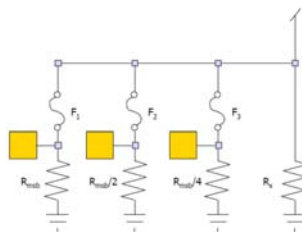


## Trimming and calibration (ch. 3.3.6)

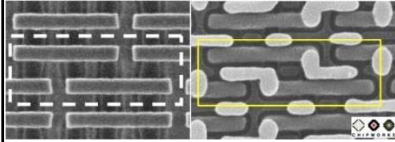

- **Systematic** variations (described in the 1st order by a **gradient**) and **random** errors in resistor values. (Picture left from <http://scsong.wordpress.com/2009/10/13/intels-32-nm-clarkdale-shows-many-changes/>)
- **Monte Carlo** simulations to see variance.
- Local fluctuations are unpredictable and cannot be (fully) compensated for with layout strategies.
- Effects of systematic errors cannot be completely cancelled, so that the global accuracy can end up being inadequate for the application at hand.
- Possible solution: **Trimming** (laser adjustment) or **electronic calibration** of (thin film) resistors.
- Or **fuses** and anti-fuses. (Fig. From [www.eng.yale.edu/elab/eeng427/lectures/EENG427106a/layout.pdf](http://www.eng.yale.edu/elab/eeng427/lectures/EENG427106a/layout.pdf))

## R-2R Resistor Ladder DAC (ch. 3.3.8)

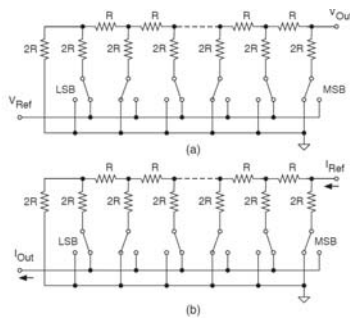

(a) Voltage mode R-2R ladder network. (b) R-2R current mode ladder networks.


- Reduces the number of resistors from  $2^n$  to  $3n$ .
- **Ex. 8 bit: 24 resistors instead of 256**
- Combines a set of signals that are related in a binary weighted fashion
- The output variable could be a voltage or a current.
- Output from R-2R in the voltage mode:

$$V_{Out} = \frac{V_{Ref}}{2}b_{n-1} + \frac{V_{Ref}}{4}b_{n-2} + \dots + \frac{V_{Ref}}{2^{n-1}}b_1 + \frac{V_{Ref}}{2^n}b_0, \quad (3.14)$$


which is the DAC conversion of a digital input  $\{b_{n-1}, b_{n-2}, \dots, b_1, b_0\}$ .

- The "Kelvin divider" is intrinsically monotonic – not the R-2R.

## R-2R Resistor Ladder DAC

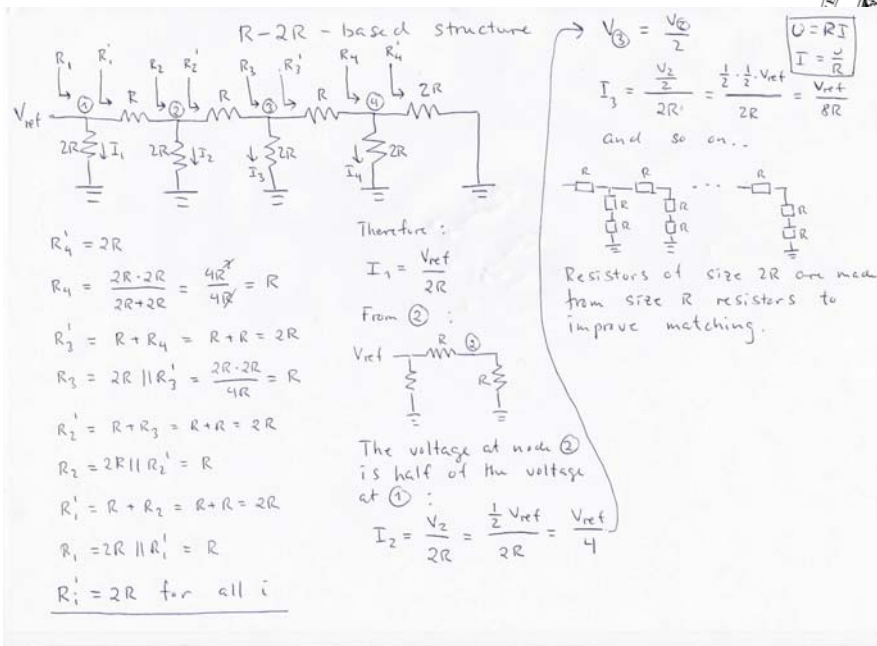

## Current-mode R-2R (ch. 3.3.8)

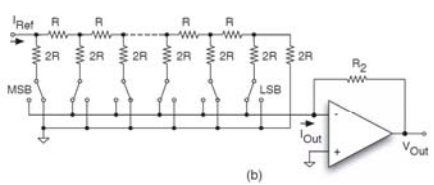

$$I_{Out} = \frac{I_{Ref}}{2} b_{n-1} + \frac{I_{Ref}}{4} b_{n-2} + \dots + \frac{I_{Ref}}{2^{n-1}} b_1 + \frac{I_{Ref}}{2^n} b_0 \quad (3.15)$$

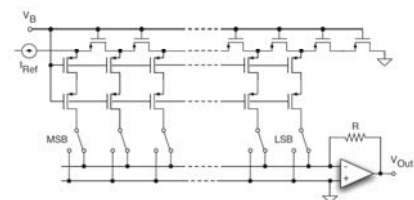


Figure 3.21. R-2R architecture with MOS transistors replacing the resistors.

- The current-mode R-2R ladder network is converted to a voltage with an operational amplifier.
- Only two resistance values  $\rightarrow$  good matching
- Impedance at virtual ground is code dependent  $\rightarrow$  code dependent amplification of the op-amp offset and its low frequency noise.
- For medium accuracy the resistors may be replaced by MOS transistors, saving area.

# Deglitching (ch. 3.3.9)

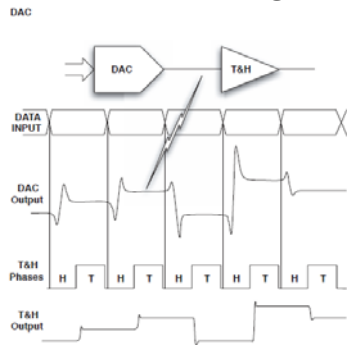


Figure 3.25. Deglitch circuit and possible voltages.

decimal	Binary k1k2k1	Thermometer code #k1k2k1k2k1k2k1
0	000	0000000
1	001	0000001
2	010	0000011
3	011	0000111
4	100	0001111
5	101	0011111
6	110	0111111
7	111	1111111

- Ideally a DAC should change from one value to its new one
- Non-synchronous switching in the R-2R network produces **glitches** that can cause **non-linearity, harmonic distortion and wasted energy**. (main source of glitches)
- Deglitching may be done by T/H (=S/H) after the DAC.
- Modify some or all of the digital word from binary to **thermometer code** (most popular)
- Exact **matching** in time (difficult)
- Reducing the bandwidth by placing **C** across Rfeedback.

# Capacitor based architectures (ch. 3.4)

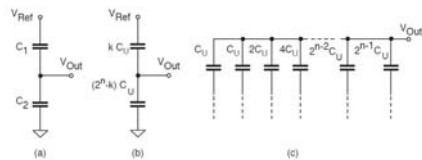


Figure 3.26. (a) and (b) Simple capacitor divider. (c) Array of binary weighted capacitors.

$$V_{Out} = V_{Ref} \frac{C_1}{C_1 + C_2} \quad (3.18)$$

- The series of two capacitors, initially discharged between  $V_{ref}$  and ground yields  $V_{Out}$  given by eq. 3.18.
- The capacitors used are **multiples** of a **unity** element.
- Capacitors made from **poly-oxide-poly** or **Metal-Insulator-Metal, MIM**.
- Fingers of metal and vias; **MMCC**


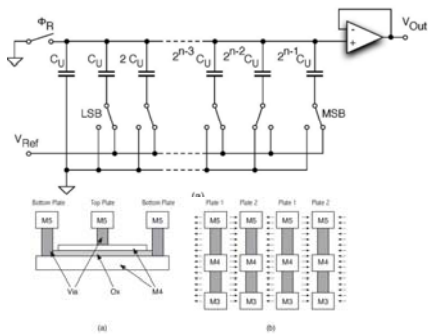


Figure 3.27. (a) MIM capacitance. (b) MMCC capacitance using three metal levels.

## Parallel charge sharing DAC principle

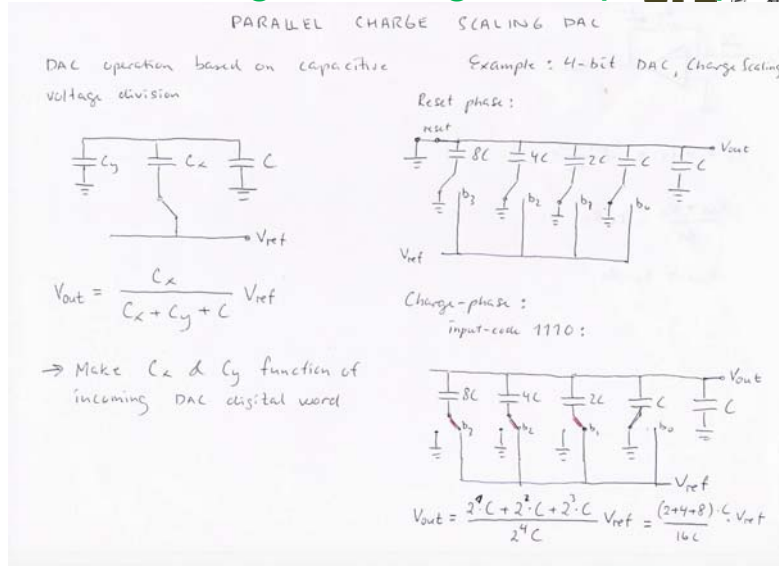

## Hybrid Capacitive-Resistive DACs (ch. 3.4.4)

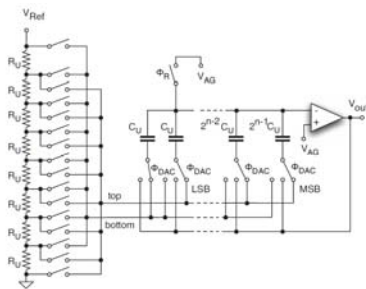


Figure 3.31. Hybrid architecture made by a Kelvin divider followed by a flip-around MDAC.

### Keep in Mind

Any capacitor-based architecture requires a reset phase to make sure that the array is initially discharged. Since the output voltage is not valid during the reset, a track and hold sustains the output.

- Resistive and Capacitive DACs may be combined to give hybrid solutions.
- Resistive DAC for coarse conversion and capacitive DAC for the fine conversion.

## Current source based architectures (ch. 3.5)


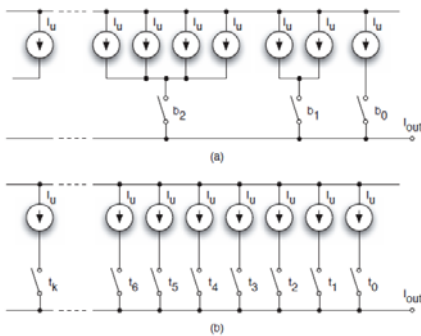


Figure 3.32. (a) Binary weighted control. (b) Unary weighted control.

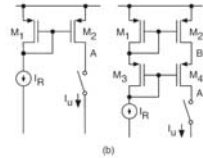An  $n$ -bit current steering DAC switches  $k$  out of  $2^n - 1$  unity current generators toward the output node under the control of the  $n$ -bit digital input.



mirror. (b) Simple and cascode MOS current

- Binary weighted current sources
  - Output current may be dumped through a resistor
  - Simple or cascode current mirrors may be used for unity current sources
  - Mismatch in the saturation current,  $I_D$ , is a source of error
- $$I_D = \beta (V_{gs} - V_{th})^2 \quad (3.29)$$
- $\Delta I/I$  halves if the gate area increases by a factor 4.

## Current sources selection (1/2) (ch. 3.5.4)

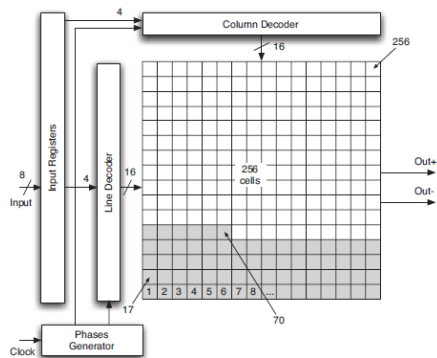


Figure 3.38. 8-bit DAC with thermometric selection of current cells.

- The **unity current sources** are often arranged in a **two-dimensional** array whose optimum shape is a square with  $2^{n/2}$  lines and columns if the number of bits  $n$  is even.
- The **simplest** thermometric selection is **sequential** by lines and columns starting from **one corner** of the array. Fig 3.38 shows the block diag. Of a possible 8-bit DAC with 70 selected cells corresponding to the input code 01000110. A possible grading error in  $x$  and  $y$  directions causes **INL**.
- Using a more complex selection technique reduces the INL. ...

## Current sources selection (2/2) (ch. 3.5.4)

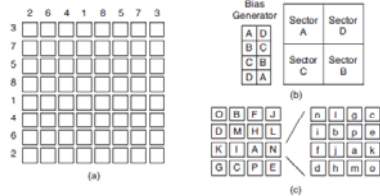



Figure 3.39. (a) Line and column shuffling. (b) Use of multiple current references for minimizing the threshold mismatch. (c) Random walk selection of unity cells.

- Using a more complex selection technique reduces the INL. ...; shuffling lines and columns to randomize the mismatches and keep the accumulated error low (Figure 3.39 a).
- The  $Q^2$  *Random Walk* method has given excellent linearity for 12-bit resolution with a reasonable silicon area.
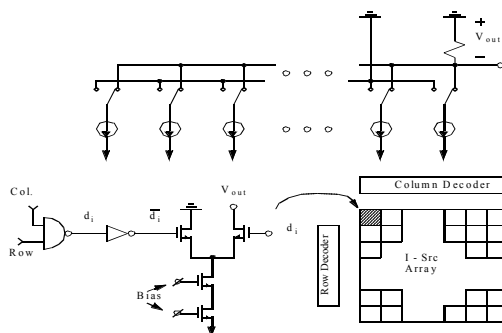
## Thermometer-code Current-Mode D/A-Converter (12.3)



- Thermometer-code** decoder in both row and column, for inherent monotonicity and good DNL
- Current is switched to the output when both row and column lines for a cell are high
- Cascode current source used for improved current matching
- Suited for high speed, with **output fed directly into a resistor** (50 or 75 Ohms), instead of an output opamp.
- The delay to all switches must be equal (suppress glitching)
- Important that the edges of  $d_i$  and  $d_i'$  are synchronized
- (From "Johns & Martin")



## A few published DACs



Publication year	SFDR @Nyquist [dB]	ENOB @ Nyquist	Nyquist update rate, [Ms/s]	Power consumpt. [mW]	Area [mm <sup>2</sup> ]	Supply voltage [V]	Technology [nm]	other	Reference
2009	>60dB	9.7	1000	188			65	Current steering	Lin et al., ISSCC '09
2008	80	12.9	11	119	0.8	1.8	180	"current steering"	Radulov, APPCAS '08
2007	59	9.5	200 @3.3 V	56	2.25	3.3	180	"current steering"	Mercer, JSSC, Aug. '07
2004	40	6	250	23	0.14	1.8	180	"binary weighted"	Deveugele, JSSC, July '04
2001	61	9.84	1000	110	0.35	3.0	350	"current steering"	Van den Bosch, JSSC, Mar. '01
1988	95	15.45	0.044	15	5	2.5-5	2000		Schouvenaars, JSSC, Dec. '88

## Litterature



- Johns & Martin: "Analog Integrated Circuit Design"
- Franco Maloberti: "Data Converters"

## Next week, 1/3:



- More on Nyquist Analog to Digital Converters (ch. 4 in "Maloberti")
- Messages are given on the INF4420 homepage.
- Questions: [sa@ifi.uio.no](mailto:sa@ifi.uio.no) , 22852703 / 90013264