

Q.1 (Example 12.1 of J&Ks')

Show that an estimate of the time constant for a network of n resistors, each of size R in series, with capacitive loading C at each node, is given by $\tau = RC \cdot (n^2/2)$. How much settling time is required for the output to settle to 0.1 percent of its final value.

Hints: Use zero-value time constant technique and assume a dominating pole exists.

The dominant-pole approximation is useful when a dominant pole exists. In some circuits, it may not be the case and zero-value time-constant analysis is used to estimate the **worst-case** -3dB frequency.

The procedure to find out the -3dB frequency of a given circuit is listed below:

1. Identity important capacitors and neglect all small capacitors. If not possible, consider all capacitors.
2. For each identified capacitor C_i , calculate the equivalent resistance R_i **seen by** C_i by
 - Shorting all independent voltage sources
 - Opening all independent current sources
 - Setting all other capacitors to zero (i.e. circuit-opening all other capacitors)
3. Calculate individual time constant τ_i contributed by each capacitor C_i using $\tau_i = R_i C_i$.
4. Approximate the -3dB bandwidth by

$$\omega_{-3\text{dB}} = \frac{1}{\sum R_i C_i}$$

Copy from HKUST ELEC304 Lecture notes 2003 by Alex Leung.

Q.2 (12.8 of J&Ks')

Consider an n -bit DAC built using binary-weighted capacitors (shown in Fig. 1), where capacitor tolerances are ± 0.5 percent. What would be the worst-case differential nonlinearity in units of LSBs, and at what transition does it occur?

 


Fig. 1 (Fig. 3.28a in Maloberti's book)

Q.2 (12.8 of J&Ks')

For the 4-b R-2R DAC shown below, what is the output error (in LSBs) when $R_A = 2.01 R_B$? What is the output error when $R_C = 2.01 R$?

