

Nº 13.1 (#31.36)

$$\begin{aligned}
 V_0 &= 120 \text{ V} \\
 L &= 0.28 \text{ H} \\
 C &= 4 \mu\text{F} \\
 I_0 &= 1.7 \text{ A}
 \end{aligned}$$

SI
 $4 \cdot 10^{-6} \text{ F}$

a) Impedance of RLC-circuit is defined as

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

There is resonance in the circuit when impedance is minimal (we get maximal current):

So, Z is minimal when reactances are equal

$$X_L = X_C$$

Where inductive reactance is

$$X_L = \omega L$$

and capacitive reactance is

$$X_C = \frac{1}{\omega C}$$

We obtain the following equation for resonance frequency:

$$\omega_0 L = \frac{1}{\omega_0 C}$$

that gives

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{or} \quad \omega_0 = \frac{1}{\sqrt{0.28 \text{ H} \cdot 4 \cdot 10^{-6} \text{ F}}} \approx \underline{945 \text{ s}^{-1}}$$

b) Current in RLC-circuit is defined by the impedance:

$$I_0 = \frac{V_0}{Z}, \quad \text{where } Z = Z(\omega).$$

At resonance we have:

$$Z_0 = Z(\omega_0) = \sqrt{R^2 + \left(\omega_0 L - \frac{1}{\omega_0 C}\right)^2} = \sqrt{R^2 + \left(\sqrt{\frac{L}{C}} - \sqrt{\frac{L}{C}}\right)^2} = R$$

Therefore active resistance is

$$\underline{R = Z_0 = \frac{V_0}{I_0}} \Rightarrow \underline{R = \frac{120 \text{ V}}{1.7 \text{ A}} \approx \underline{70.6 \Omega}}$$

c) Voltage over coil and ~~capacitor~~ capacitor depends on ~~it~~ their reactances (for resistor we can use usual resistance):

$$I_C = \frac{V_C}{X_C} ; I_L = \frac{V_L}{X_L} ; I_R = \frac{V_R}{R}$$

The elements are in series in the LRC-circuit, so

$$I_L = I_C = I_R = I_0$$

The reactances are equal at resonance:

$$X_L^\circ = X_C^\circ = \frac{1}{\omega_0 C} = \sqrt{\frac{L}{C}} \quad \text{or} \quad X_L = X_C = \sqrt{\frac{0.28 \text{ H}}{4 \cdot 10^{-6} \text{ F}}} \approx 264.6 \Omega \approx 265 \Omega$$

That gives the voltage:

$$V_C = I_0 X_C^\circ = I_0 \sqrt{\frac{L}{C}}$$

$$\Rightarrow V_L = V_C = 1.7 \text{ A} \cdot 265 \Omega \approx \underline{450 \text{ V}}$$

$$V_L = I_0 X_L^\circ = I_0 \sqrt{\frac{L}{C}}$$

We can see that at resonance voltage ^{amplitude} over capacitor and coil is bigger than voltage of source!


Voltage of the resistor is

$$\underline{V_R} = I_0 \cdot R \Rightarrow \underline{V_R} = 1.7 \text{ A} \cdot 70.6 \Omega \approx \underline{120 \text{ V}}$$

Note: Voltages over the capacitor and coil are shifted with opposite phase, so their total contribution is zero at resonance.

R, L, C
 V_{in}, ω
 $V_{out} - ?$
 V_{in}

The sketch of the problem

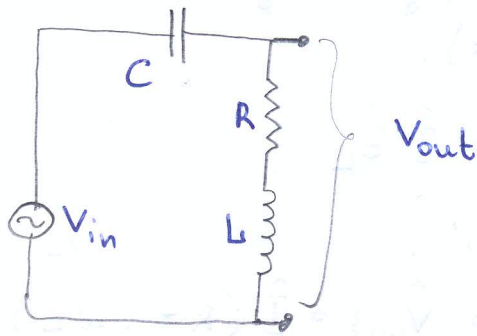

a) In order to define V_{out} we can use complex reactance of the elements in the circuit:

$$\hat{Z}_R = R \quad - \text{real}$$

$$\hat{Z}_L = i\omega L = iX_L; \quad \hat{Z}_C = \frac{X_C}{i} = -iX_C = \frac{1}{i\omega C}$$

The elements R, L and C are in series, so the total impedance

$$\hat{Z} = \hat{Z}_C + \hat{Z}_R + \hat{Z}_L$$

$$\Rightarrow \hat{Z} = R + i(X_L - X_C)$$

Therefore the impedance (its real value, that corresponds to relation of current and voltage amplitudes):

$$Z = \text{Re. } \hat{Z} = \sqrt{\hat{Z} \hat{Z}^*} = \sqrt{(R + i(X_L - X_C))(R - i(X_L - X_C))}$$

$$\Rightarrow Z = \sqrt{R^2 + (X_L - X_C)^2}$$

So the magnitude of the current through the circuit is

$$I = \frac{V_{in}}{Z} \quad \Rightarrow \quad I = \frac{V_{in}}{\sqrt{R^2 + (X_L - X_C)^2}}$$

Or in complex form (when we keep phase):

$$\hat{I} = \frac{\hat{V}_{in}}{\hat{Z}} \quad \Rightarrow \quad \hat{I} = \frac{\hat{V}_{in}}{R + i(X_L - X_C)}$$

Voltage across R and L - elements is

$$\hat{V}_{out} = \hat{V}_R + \hat{V}_L$$

where \hat{V}_R, \hat{V}_L are complex voltages across the resistor and solenoid.

(Note: we should use complex voltage in general case, because we have to include phase ~~shift~~).

$$\hat{V}_R = \hat{I} \hat{Z}_R \quad \text{and} \quad \hat{V}_L = \hat{I} \hat{Z}_L$$

Therefore:

$$\hat{V}_{out} = \hat{I} (\hat{Z}_R + \hat{Z}_L) \Rightarrow \hat{V}_{out} = \hat{I} (R + i\omega L)$$

or for the magnitudes:

$$V_{out} = I \cdot \sqrt{R^2 + X_L^2}$$

Finally we obtain that

$$\hat{V}_{out} = \hat{V}_{in} \frac{\hat{Z}_R + \hat{Z}_L}{\hat{Z}} = \hat{V}_{in} \frac{\hat{Z}_R + \hat{Z}_L}{\hat{Z}_R + \hat{Z}_L + \hat{Z}_C} = \frac{\hat{V}_{in}}{1 + \frac{\hat{Z}_C}{\hat{Z}_R + \hat{Z}_L}}$$

or in explicit form:

$$\hat{V}_{out} = \frac{\hat{V}_{in}}{1 - \frac{iX_C}{R + iX_L}} = \frac{\hat{V}_{in}}{1 - i \frac{1/\omega C}{R + i\omega L}}$$

For magnitude we have:

$$V_{out} = V_{in} \frac{|\hat{Z}_R + \hat{Z}_L|}{Z} = V_{in} \frac{\sqrt{R^2 + X_L^2}}{\sqrt{R^2 + (X_L - X_C)^2}}$$

The relation is


$$\frac{V_{out}}{V_{in}} = \sqrt{\frac{R^2 + X_L^2}{R^2 + (X_L - X_C)^2}} = \sqrt{\frac{R^2 + \omega^2 L^2}{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

or by introducing

$$\omega_0 = \frac{1}{\sqrt{CL}} \Rightarrow \frac{V_{out}}{V_{in}} = \sqrt{\frac{R^2 + \omega^2 L^2}{R^2 + (\omega L)^2 (1 - \frac{\omega_0^2}{\omega^2})^2}}$$

In case when R is small:

$$\left. \frac{V_{out}}{V_{in}} \right|_{R \approx 0} = \frac{1}{|1 - \frac{\omega_0^2}{\omega^2}|} = \frac{\omega^2}{|\omega^2 - \omega_0^2|}$$

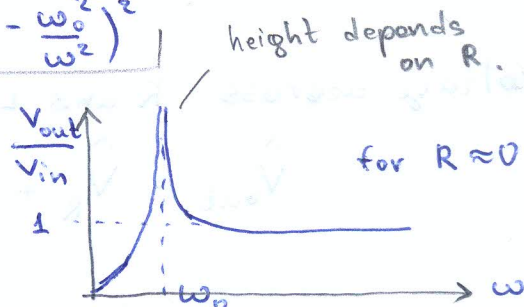

b) For low frequency : $\omega \rightarrow 0$:

$$\left. \frac{V_{out}}{V_{in}} \right|_{\omega \rightarrow 0} = \lim_{\omega \rightarrow 0} \sqrt{\frac{R^2 + \omega^2 L^2}{R^2 + \frac{\omega^2 L^2}{\omega^2 C^2} (\omega^2 - \omega_0^2)^2}} =$$



$$\approx \lim_{\omega \rightarrow 0} \omega \sqrt{\frac{R^2 + \omega^2 L^2}{R^2 + \omega^2 + L^2 (\omega^2 - \omega_0^2)^2}} = \lim_{\omega \rightarrow 0} \omega \cdot \sqrt{\frac{R^2}{L^2 \omega^4}} = 0$$

c) For high frequency : $\omega \rightarrow \infty$ ($\omega \gg \omega_0$) :

$$\left. \frac{V_{out}}{V_{in}} \right|_{\omega \rightarrow \infty} = \lim_{\omega \rightarrow \infty} \sqrt{\frac{R^2/\omega^2 + L^2}{R^2/\omega^2 + L^2 (1 - \frac{\omega_0^2}{\omega^2})^2}} = \sqrt{\frac{L^2}{L^2}} = 1.$$

Therefore we have high-pass filter with corner frequency is

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

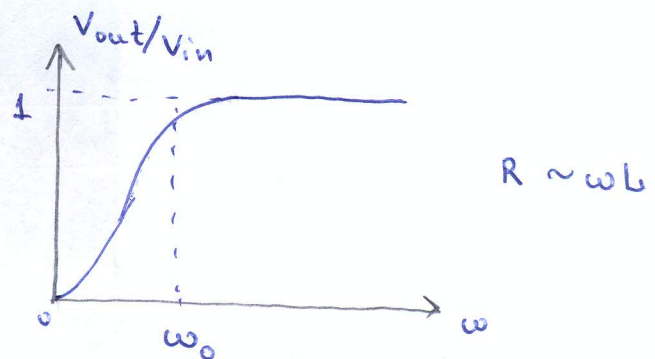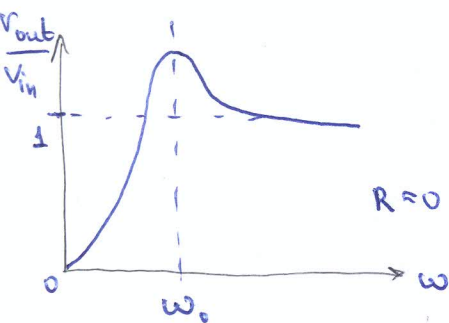

$$\begin{aligned} \varphi &= 54^\circ \\ X_c &= 350 \Omega \\ R &= 180 \Omega \\ \bar{P} &= 140 \text{ W} \end{aligned}$$

$$\begin{aligned} X_L &= ? \\ I_{\text{rms}} &= ? \\ V_{\text{rms}} &= ? \end{aligned}$$

$N = 13.3$ (#31.59)

S I

$\frac{54^\circ}{180^\circ} \pi = 0.3 \pi$ a) Phase angle of RLC-circuit is given by

$$\tan \varphi_0 = \frac{X_L - X_c}{R}$$

That gives

$$X_L = X_c + \tan \varphi_0 \cdot R$$

where φ_0 is phase angle when voltage leads current. But in our case current leads the voltage (the voltage lags the current), so φ_0 is negative!

$$\varphi_0 = -\varphi \Rightarrow \tan \varphi_0 = -\tan \varphi$$

Therefore:

$$\boxed{X_L = X_c - R \cdot \tan \varphi}$$

and $X_L < X_c$

or numerical value: is

$$\underline{X_L} = 350 \Omega - 180 \Omega \cdot \underbrace{\tan 54^\circ}_{\approx 1.376} \approx \underline{102.3 \Omega}$$

b) The mean effect is given by:

$$\bar{P} = I_{\text{rms}}^2 \cdot R$$

(because ~~only~~ resistor only consumes energy).

so

$$\boxed{I_{\text{rms}} = \sqrt{\frac{\bar{P}}{R}}} \quad \text{or} \quad \underline{I_{\text{rms}}} = \sqrt{\frac{140 \text{ W}}{180 \Omega}} \approx \underline{0.882 \text{ A}}$$

c) On the other hand the mean effect is

$$\bar{P} = V_{\text{rms}} \cdot I_{\text{rms}} \cdot \cos \varphi$$

where $\cos \varphi$ is power factor of the circuit. That gives

$$V_{\text{rms}} = \frac{\bar{P}}{I_{\text{rms}} \cdot \cos \varphi}$$

$$\text{or} \quad \boxed{V_{\text{rms}} = \frac{1}{\cos \varphi} \sqrt{\bar{P} R}}$$

Or

$$\underline{V_{\text{rms}}} = \frac{1}{\cos 54^\circ \approx 0.588} \sqrt{140 \text{ W} \cdot 180 \Omega} \approx \underline{270 \text{ V}}$$

$$d\vec{E} = (\vec{v} \times \vec{B}) d\vec{l}$$

$$F_M = q(\vec{v} \times \vec{B})$$


$$F_E = q\vec{E}$$

R, ω, B | a) In order to define emf we can use Faraday's law

$\mathcal{E} = ?$

$$\mathcal{E} = - \frac{d\Phi}{dt}$$

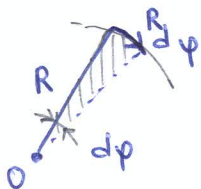by considering imaginary loop during rotation of the disk



In time dt area of the loop changes on

$$dA = \frac{1}{2} R \cdot R d\phi \quad \text{- area of triangle}$$

Therefore the magnitude of emf is

$$\mathcal{E} = \left| \frac{d\Phi}{dt} \right| = \left[d\Phi = B \cdot dA \right] = B \frac{dA}{dt} \quad \text{- for } B = \text{const.}$$

so

$$\mathcal{E} = B \cdot \frac{dA}{dt} = \frac{1}{2} B R^2 \cdot \underbrace{\frac{d\phi}{dt}}_{\omega} = \underline{\underline{\frac{1}{2} B R^2 \omega}}$$

b) The same result can be obtained by considering magnetic force :

$$d\vec{E} = (\vec{v} \times \vec{B}) d\vec{l} \quad \text{- for each segment}$$


that gives finally ($v = \omega r$)

$$\underline{\underline{\mathcal{E}}} = B\omega \int_0^R r \cdot dr = \underline{\underline{\frac{1}{2} B\omega R^2}}, \quad \text{see \#11.3}$$

c) Due to energy conservatio law we must provide the same energy that is consumed by the resistor.

Due to Ohm's law:

$$I = \frac{\mathcal{E}}{R_{\Omega}}$$

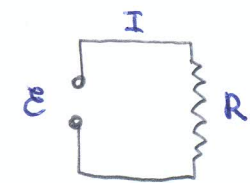

So the dissipated energy in the resistor per second is

$$P_{\mathcal{E}} = I^2 R_{\Omega} = \frac{\mathcal{E}^2}{R_{\Omega}}$$

Therefore we must provide the mechanical power is

$$\underline{\underline{P_M}} = P_{\mathcal{E}} = \frac{\mathcal{E}^2}{R_{\Omega}} = \frac{1}{2} \frac{B^2 \omega^2 R^4}{R_{\Omega}}$$