

IN4180 - Analog Microelectronics Design


Basic Operational Amplifier Design and Compensation - Part 2

Compensation and stability

Kristian G. Kjelgård and Dag T. Wisland




CMOS OPAMP topology

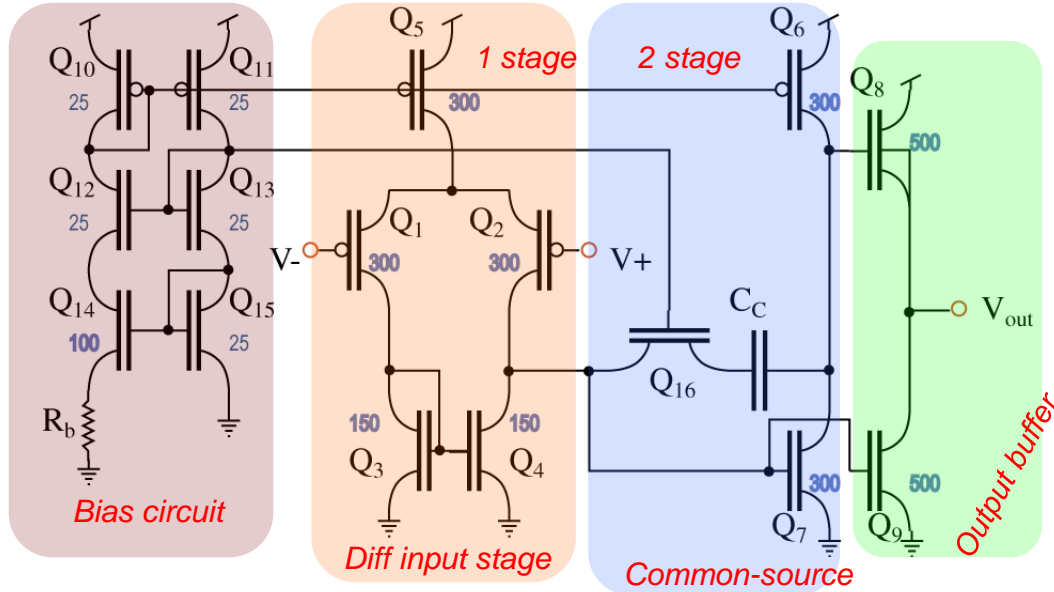

- PMOS diff input stage
- Numbers realistic transistor widths
 - Length 1-2 times minimum
- Output buffer may not be needed for capacitive loads

Two stage opamp gain

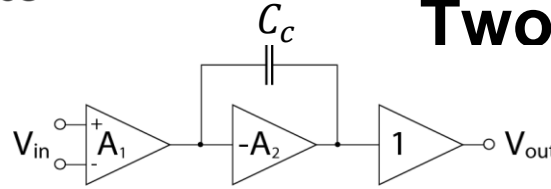

- Gain for diff pair – 1. stage

$$A_{v1} = g_{m1}(r_{ds2} || r_{ds4})$$

- Typical gain 50-100

- Gain of common source – 2. stage

$$A_{v2} = -g_{m7}(r_{ds6} || r_{ds7})$$

- Typical gain 50-100

- Gain of source follower – output buffer

$$A_{v3} = \frac{g_{m8}}{G_L + g_{m8} + g_{s8} + g_{ds8} + g_{ds9}}$$

- Gain ≈ 1
- Not needed for capacitive loads

$$g_{m1} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \sqrt{2\mu_n C_{ox} \frac{W}{L} \frac{I_{bias}}{2}}$$

$$\lambda$$

$$= \frac{k_{ds}}{2L\sqrt{V_{DS} - V_{eff} + \Phi_0}}$$

$$k_{ds} = \sqrt{\frac{2K_s \epsilon_0}{qN_A}}$$


$$r_{ds} \cong \frac{1}{\lambda I_D \gamma g_m}$$

$$g_{s8} = \frac{1}{2\sqrt{V_{SB} + |2\phi_F|}}$$

Frequency response – First order model

Midband frequencies

- C_{eq} dominates

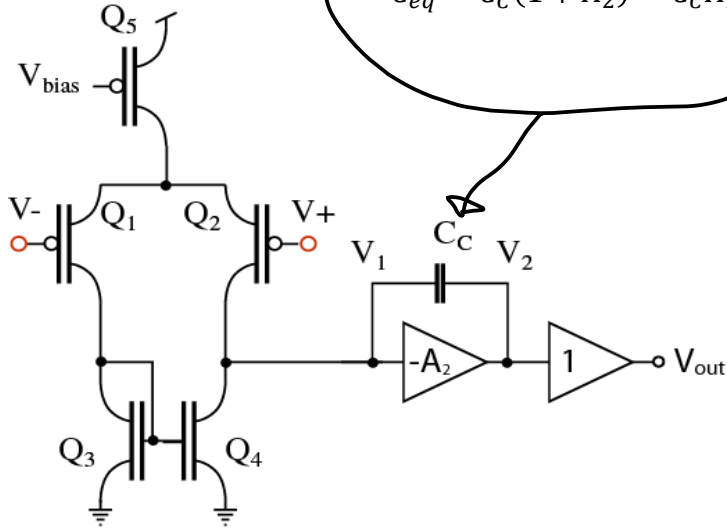

$$C_{eq} = C_C(1 + A_2) \approx C_C A_2$$

$$A_1 = g_{m1} Z_{out1} = g_{m1} \left(r_{ds2} || r_{ds4} || \frac{1}{sC_{eq}} \right)$$

at midband freq C_{eq} dominates

$$A_1 = g_{m1} \frac{1}{sC_{eq}} = g_{m1} \frac{1}{sC_C A_2}$$


$$A_v = \frac{v_{out}}{v_{in}} = A_1 A_2 A_3 \approx g_{m1} \frac{1}{sC_C A_2} \cdot A_2 \cdot 1 = \frac{g_{m1}}{sC_C}$$

Unit-gain frequency proportional to g_m assuming $A_3=1$




setting $|A_v(j\omega_{ta})| = 1$ and solve

$$\omega_{ta} = \frac{g_{m1}}{C_C} = \frac{I_{D5}}{V_{eff1} C_C}$$


Feedback stability

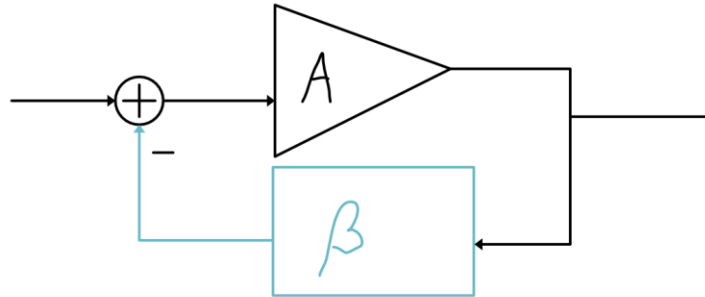

Feedback stability

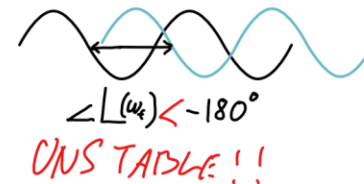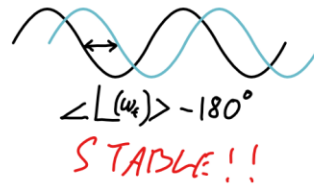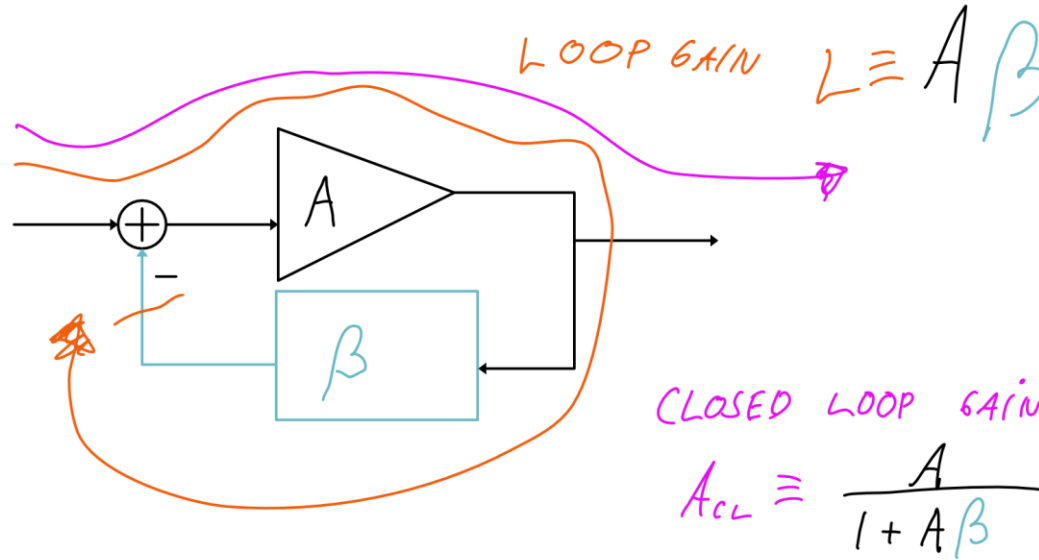


Frequency response - First order model

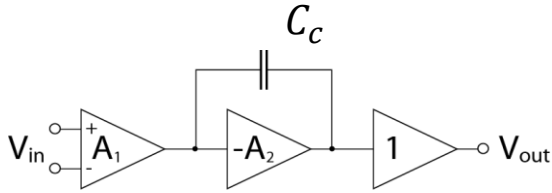


Midband frequencies

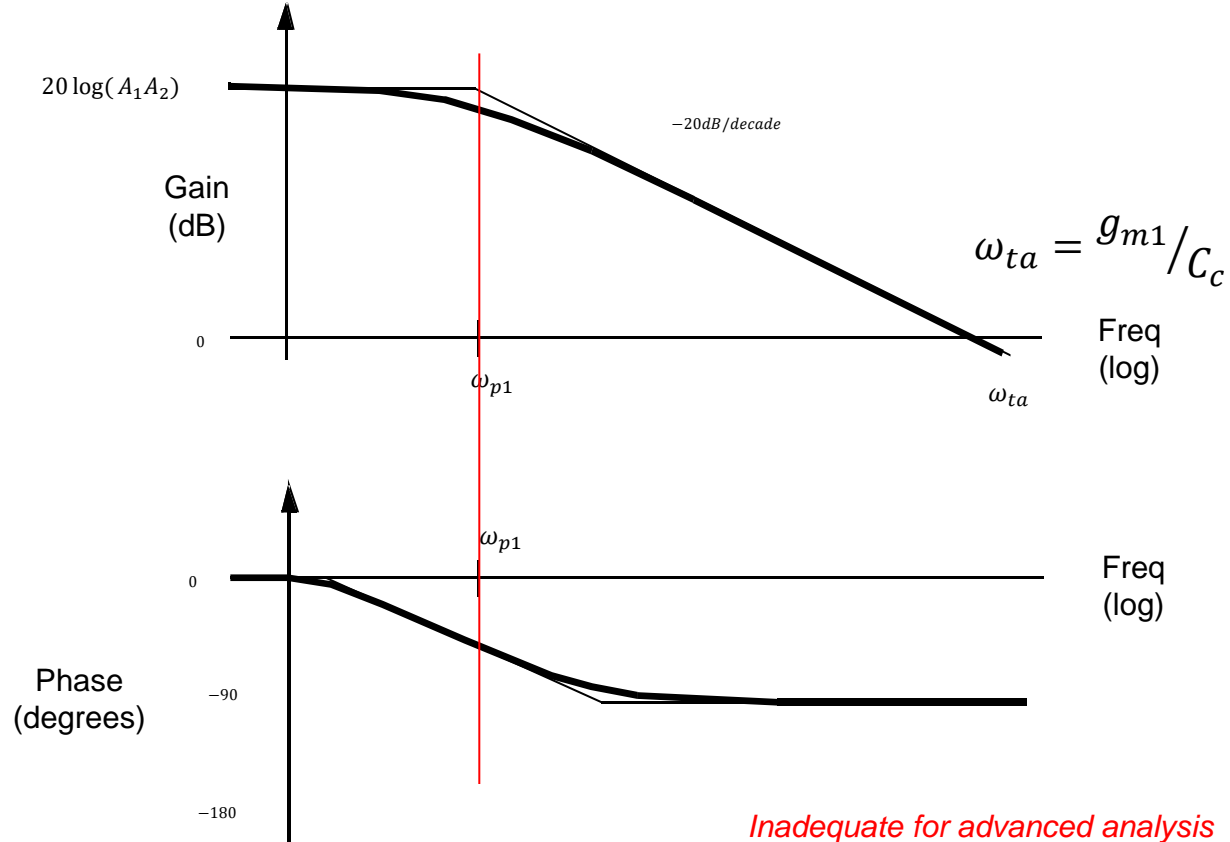- Below unit-gain frequency
- Above frequencies without compensation effects
- Ignore all C except C_c
- Ignore R_c which only has effect at ω_{ta}




Inadequate for advanced analysis

Frequency response Second order model

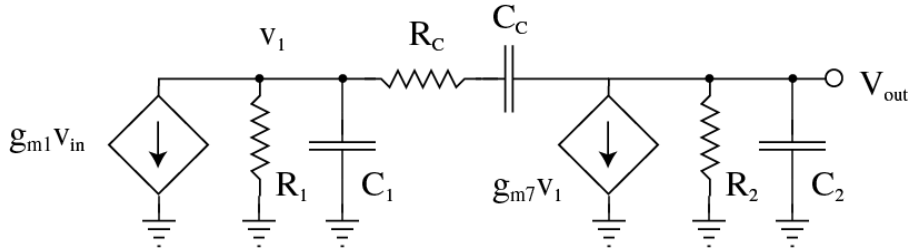

$$R_1 = r_{ds4} || r_{ds2} \text{ and } C_1 = C_{db2} + C_{db4} + C_{gs7}$$

$$R_2 = r_{ds6} || r_{ds7} \text{ and } C_2 = C_{db7} + C_{db6} + C_{L2}$$

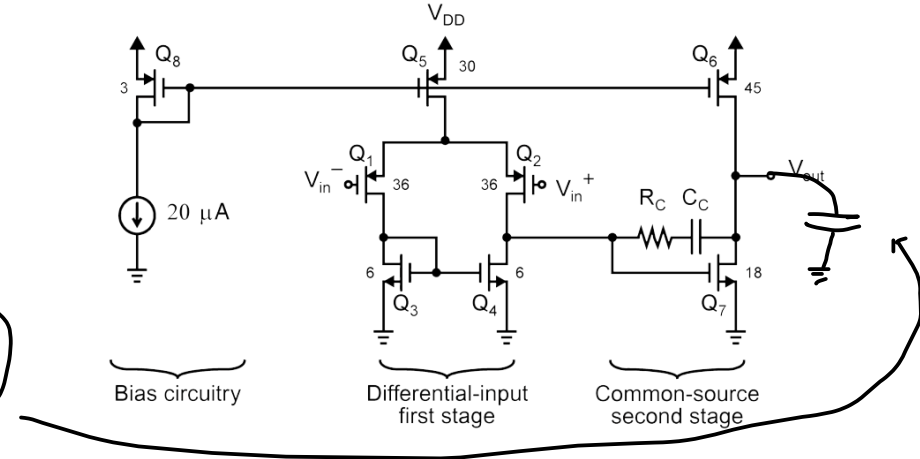

- Assume $R_C=0$ give transfer function

$$\frac{v_{out}}{v_{in}} = \frac{g_{m1}g_{m7}R_1R_2 \left(1 - \frac{sC_C}{g_{m7}}\right)}{1 + sa + s^2b}$$

$$a = (C_1 + C_C)R_2 + (C_1 + C_C)R_1 + g_{m7}R_1R_2C_C$$

$$b = R_1R_2(C_1C_2 + C_1C_C + C_2C_C)$$

- Assume widely separated poles

$$D(s) = \left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \approx 1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1}\omega_{p2}}$$

- Dominant pole

$$\begin{aligned} \omega_{p1} &= \frac{1}{R_1[C_1 + C_C(1 + g_{m7}R_2)] + R_2(C_1 + C_C)} \\ &\approx \frac{1}{R_1C_C(1 + g_{m7}R_2)} \\ &\approx \frac{1}{g_{m7}R_1R_2C_C} \end{aligned}$$

- Non-dominant pole

$$\begin{aligned} \omega_{p2} &= \frac{g_{m7}C_C}{C_1C_2 + C_1C_C + C_2C_C} \\ &\approx \frac{g_{m7}}{C_1 + C_2} \end{aligned}$$

- Increasing g_{m7}
→ increased pole distance
- Pole splitting compensation
- C_C may decrease ω_{p1}

- Additional zero

I use $\beta = 1$ (max feedback) in this analysis

$$\frac{v_{out}}{v_{in}} = \frac{g_{m1}g_{m7}R_1R_2 \left(1 - \frac{sC_C}{g_{m7}}\right)}{1 + sa + s^2b} \quad \Rightarrow \quad \omega_z = -\frac{g_{m7}}{C_C}$$

- Right half-plane → negative phase shift with decreased PM
- Stability issues
 - Hard to get rid of, but pole distance is increased with g_{m7}

- Have to make $R_C > 0$

- Zero with some resistive element

$$\omega_z = -\frac{1}{C_C(1/g_{m7} - R_C)}$$

- May eliminate that zero by setting

$$R_C = \frac{1}{g_{m7}}$$

- Alternatively try to cancel ω_{p2} with ω_z

$$\frac{g_{m7}}{C_1 + C_2} = -\frac{1}{C_C(1/g_{m7} - R_C)} \Rightarrow R_C = \frac{1}{g_{m7}} \left(1 + \frac{C_1 + C_2}{C_C}\right)$$


- “Overcompensation” might even be wise:

$$\omega_z = 1.7\omega_t$$

$$R_C \gg 1/g_{m7} \Rightarrow \omega_z \approx \frac{1}{R_C C_C} \quad \omega_t \approx g_{m7}/C_C \text{ gives } R_C = \frac{1}{1.7g_{m7}}$$

Two-pole amplifier


- Dominant poles of two-stage amps

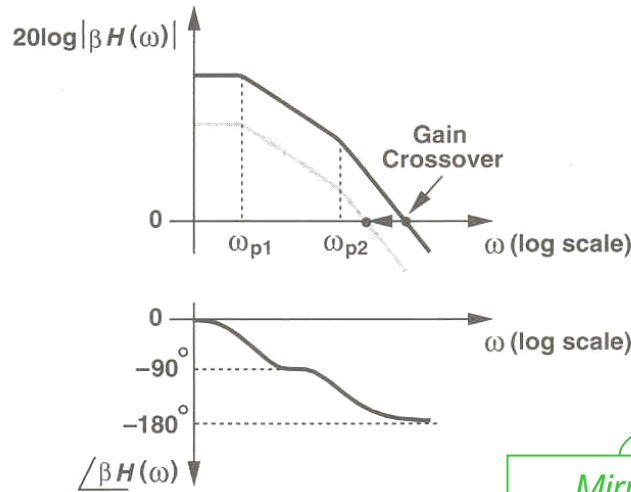

– 1. stage

- High gain
- Dominant pole at output

Mirror pole

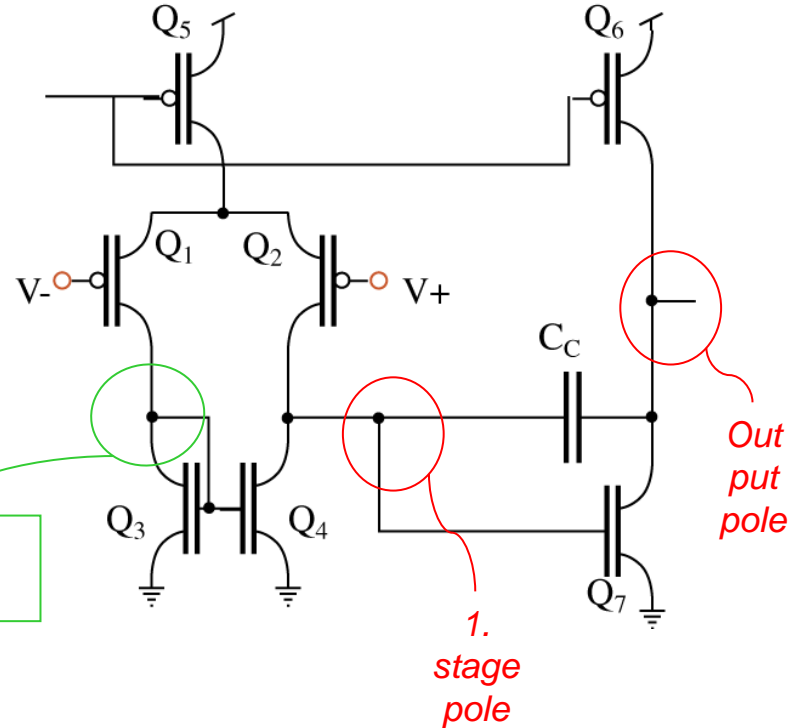

General form:

$$A_v(s) = \frac{N}{D} \quad \begin{array}{l} \text{ZEROS} \\ \text{POLES} \end{array} = \frac{A_0 \left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

From two-stage second order analysis:

$$A(s) = \frac{V_{out}}{V_{in}} = \frac{-g_m R_2 \left(1 + s \frac{C_{GD}}{g_{m1}}\right)}{1 + sa + s^2 b}$$


$$a = R_s [C_{GS1} + C_{GD1} (1 + g_{m1} R_2)] + R_2 (C_{GD1} + C_2)$$

$$b = R_s R_2 (C_{GD1} C_{GS1} + C_{GS1} C_2 + C_{GD1} C_2)$$

$$\omega_{p1} = \frac{1}{g_m R_1 R_2 C_c}$$

$$\omega_{p2} = \frac{g_{m2}}{C_1 + C_2}$$


$$\omega_z = -\frac{g_{m2}}{C_c}$$

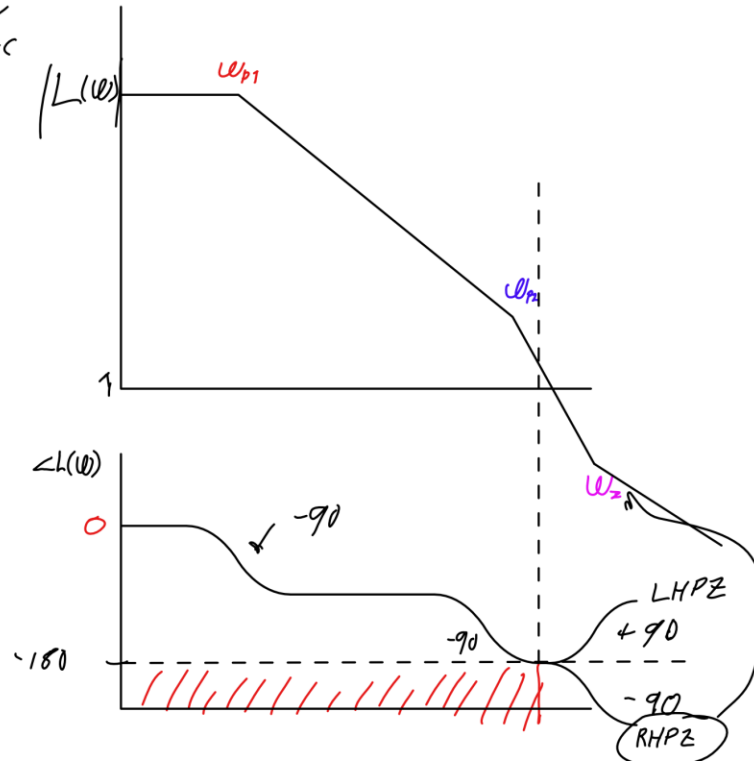

Opamp compensation

- Dominant-pole compensation
 - Forcing a feedback system to have 1. order response up to loop unit-gain frequency ω_t
 - First order system unconditional stable with > 90 phase margin
- Lead compensation
 - Adding zero, ω_z , just above ω_t
 - May improve PM with 20°

Dominant pole comp using miller Cc

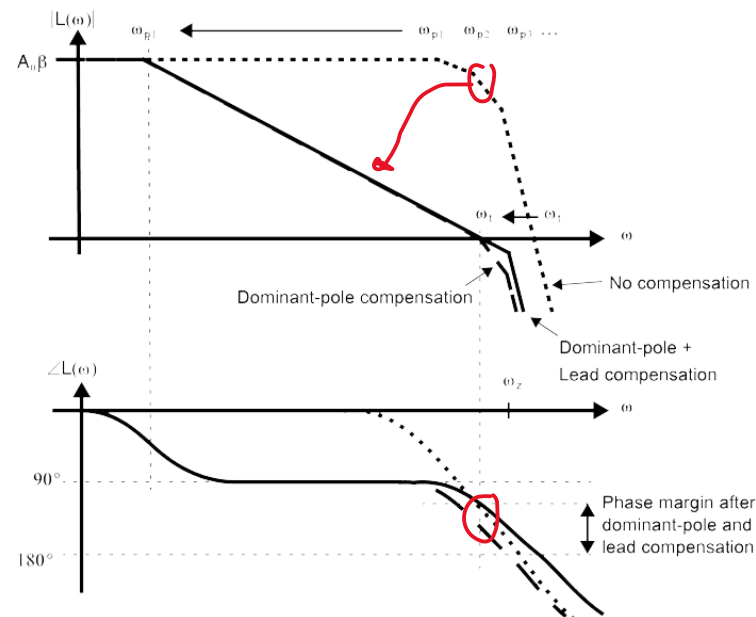

Lead comp using R_c

Compensation procedure

Dominant pole


- From first order model C_C and ω_t is given as:

$$\omega_t = L_0 \omega_{p1} = \beta \frac{g_{m1}}{C_C}$$

- Find C_C

$$C'_C = \left(\beta \frac{g_{m1}}{g_{m7}} \right) C_L$$

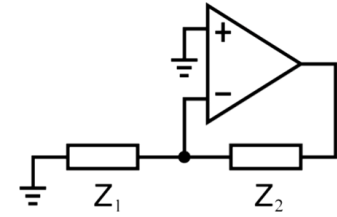setting unit-gain frequency close to second pole



$$L(s) \approx A(s) \frac{Z_1}{Z_1 + Z_2}$$

$$\beta = \frac{Z_1}{Z_1 + Z_2}$$

Two stage opamp small signal model

$$L(s) \approx A(s) \frac{Z_1}{Z_1 + Z_2}$$

Lead compensation - controlling Zero

$$\omega_z \approx \frac{-1}{C_C \left(\frac{1}{g_{m7}} - R_C \right)}$$

Several possibilities for R_C :


$$R_C = \frac{1}{g_{m7}} \rightarrow \omega_z = \infty$$

$$R_C > \frac{1}{g_{m7}} \quad \text{RHPZ} \rightarrow \text{LHPZ and cancel } \omega_{p2}$$

$R_C \gg \frac{1}{g_{m7}}$ Moving LHPZ to a frequency slightly higher than ω_t (wo R_C)
Recommended to get more PM (20-30 degrees)


$$\omega_{p2} = \frac{g_{m7}C_C}{C_1C_2 + C_1C_C + C_2C_C} = \frac{-1}{C_C \left(\frac{1}{g_{m7}} - R_C \right)} \Rightarrow R_C = \frac{1}{g_{m7}} \left(1 + \frac{C_1 + C_2}{C_C} \right)$$

Two stage opamp small signal model

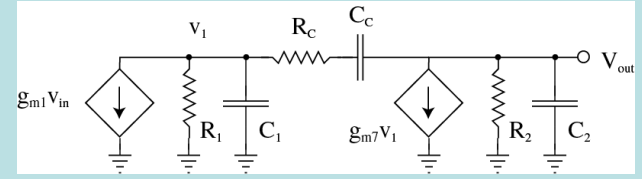

R_C as transistor

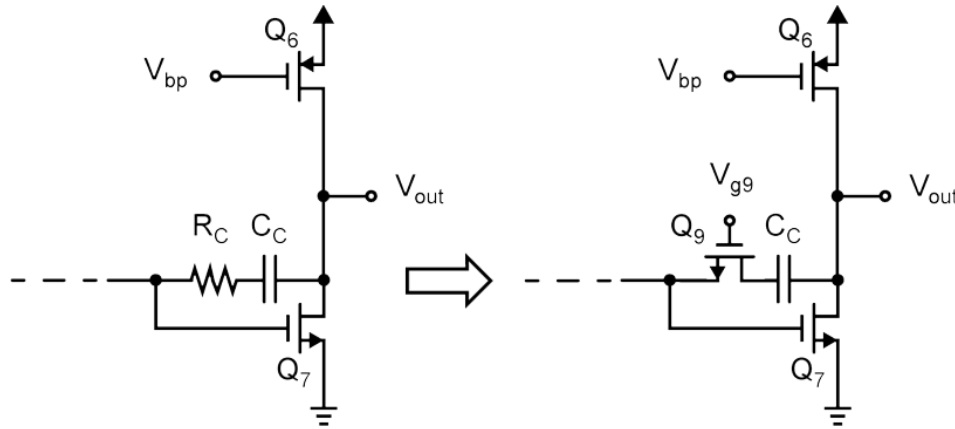
- Compensation resistor
 - Replaced by transistor in triode region



$$R_C = r_{ds} = \frac{1}{\mu_n C_{ox} \frac{W}{L} V_{eff}}$$


1. Start with $C'_C = \left(\beta \frac{g_{m1}}{g_{m7}} \right) C_L$ setting unit-gain frequency close to second pole
2. By simulation (SPICE, CADENCE) find frequency with -125° phase shift (called gain A')
- This is our unit gain frequency ω_t target
3. Choose new C_C such that ω_t is unit-gain freq of L(s)
 - $C_C = C'_C A'$ giving 55° phase margin
 - A couple of simulation iterations may be necessary
4. Choose R_C : $R_C = \frac{1}{1.7 \omega_t C_C}$ *Almost optimum lead compensation for any opamp*
 - Giving phase margin of 85° ($+30^\circ$) leaving 5° for variations

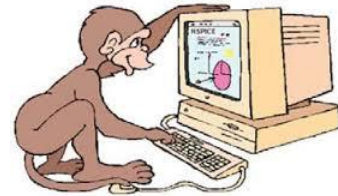1. Sometimes phase margins are not adequate, then increase C_C
2. Replace R_C with a transistor $R_C = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L} \right)_{16} V_{eff16}}$




Opamp compensation Cadence example

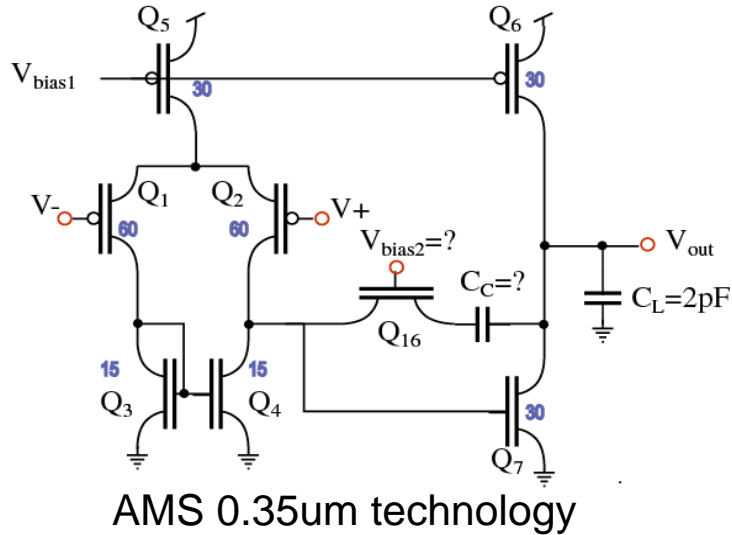- Find best compensation network C_c and R_c for:




Find bias voltage:

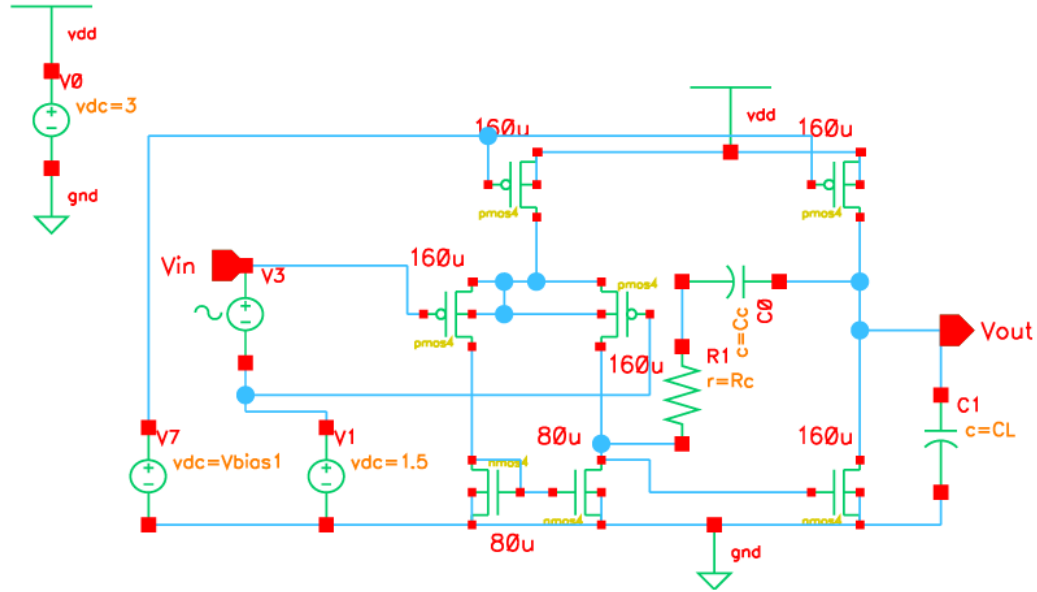

Vbias1=2.3V give 84μA tail current

Found by simple simulation run displaying tail current

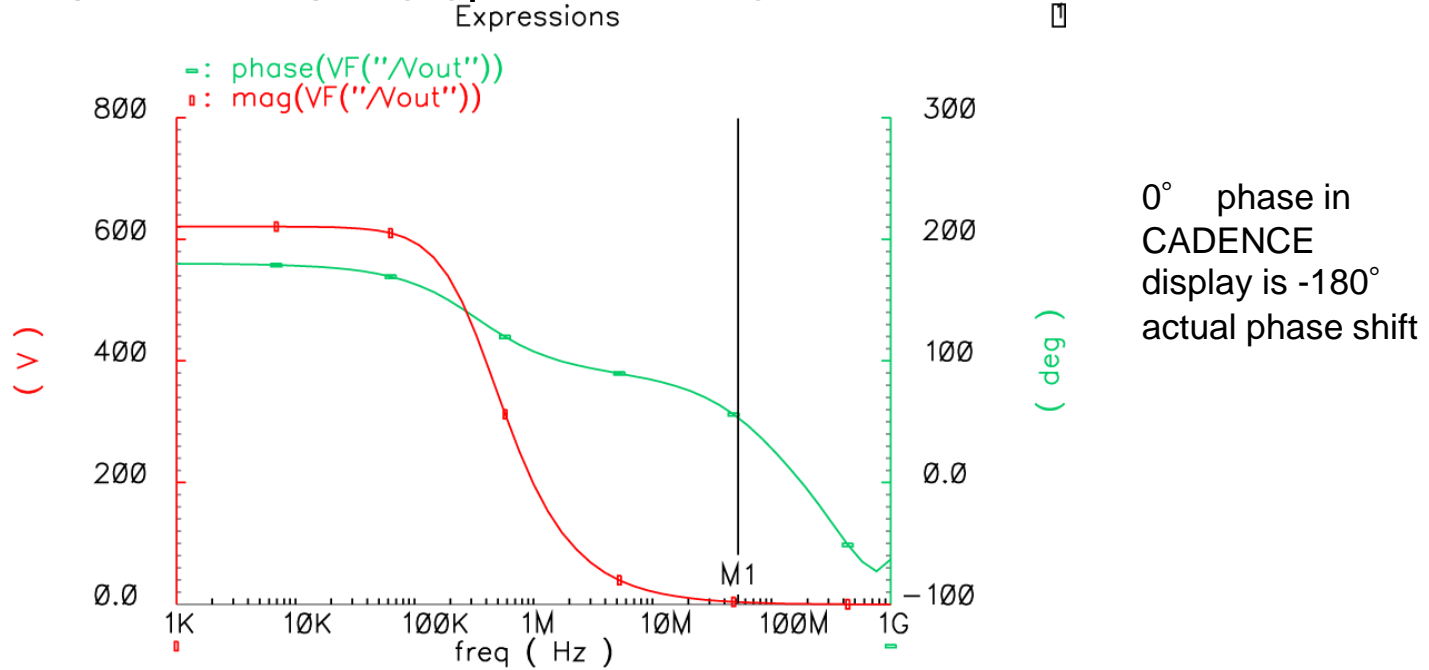- Start with $C_c=0.5\text{pF}$ and $R_c=0$



Find $(180-125)=55^\circ$ phase shift at $\omega t=50.1\text{MHz}$ with gain $A'=3.7$

$$C_c = C'_c A' = 0.5\text{pF} \cdot 3.7 \approx 1.9\text{pF}$$

- New simulation with $C_c=1.9\text{pF}$ give
 - $\omega_t=44.7\text{MHz}$ with $A'=1.32$

$$C_C = C'_C A' = 1.3\text{pF} \cdot 1.32 \approx 2.5\text{pF}$$

- New simulation with $C_c=2.5\text{pF}$ give
 - $\omega_t=41\text{MHz}$ with $A'=1.2$

$$C_C = C'_C A' = 2.5\text{pF} \cdot 1.2 \approx 3.1\text{pF}$$


- New simulation with $C_c=3.1\text{pF}$ give
 - $\omega_t=37.7\text{MHz}$ with $A'=1.00$

- Finding R_c


$$R_C = \frac{1}{1.2\omega_t C_C} = \frac{1}{1.2 \cdot 37.7 \cdot 10^6 \cdot 3.1 \cdot 10^{-12}} \approx 7132\Omega$$

Marker at
55 deg
phase
margin


- Adding compensation resistor R_c

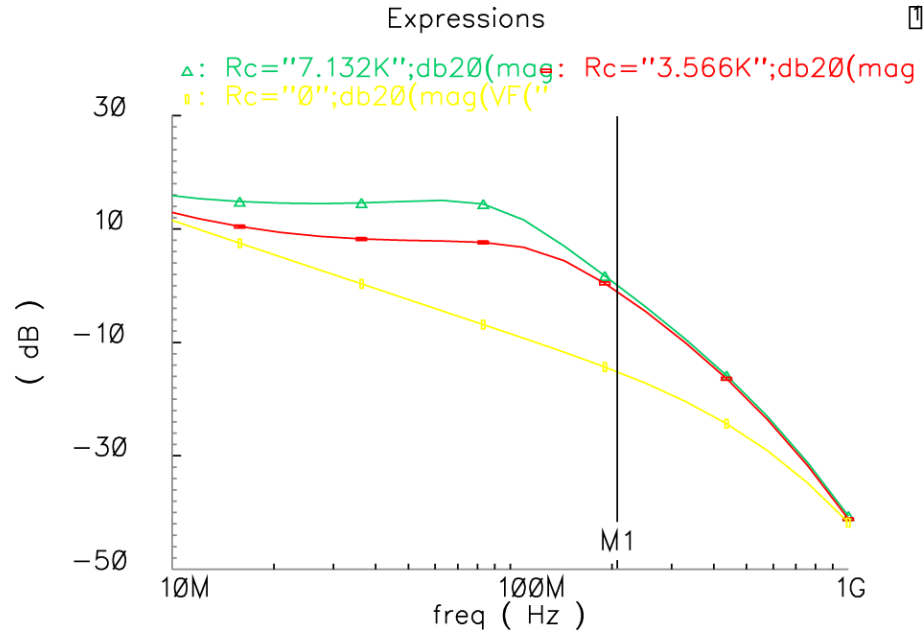


Give unit-gain freq of 209MHz

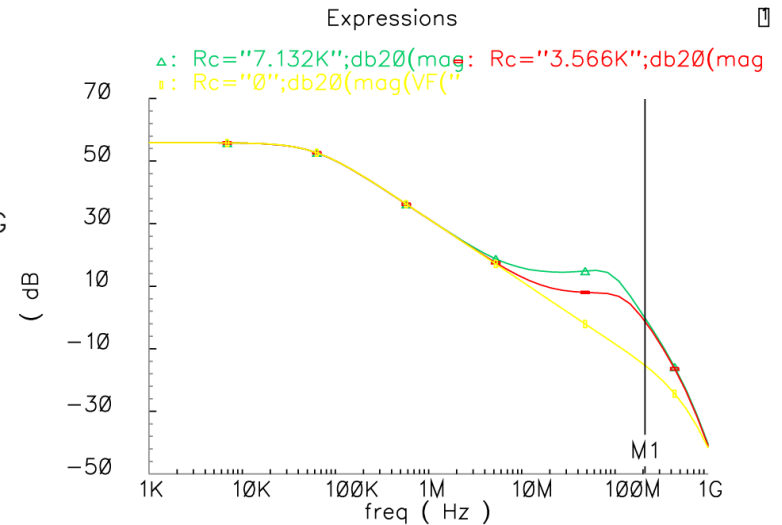

Phase margins?

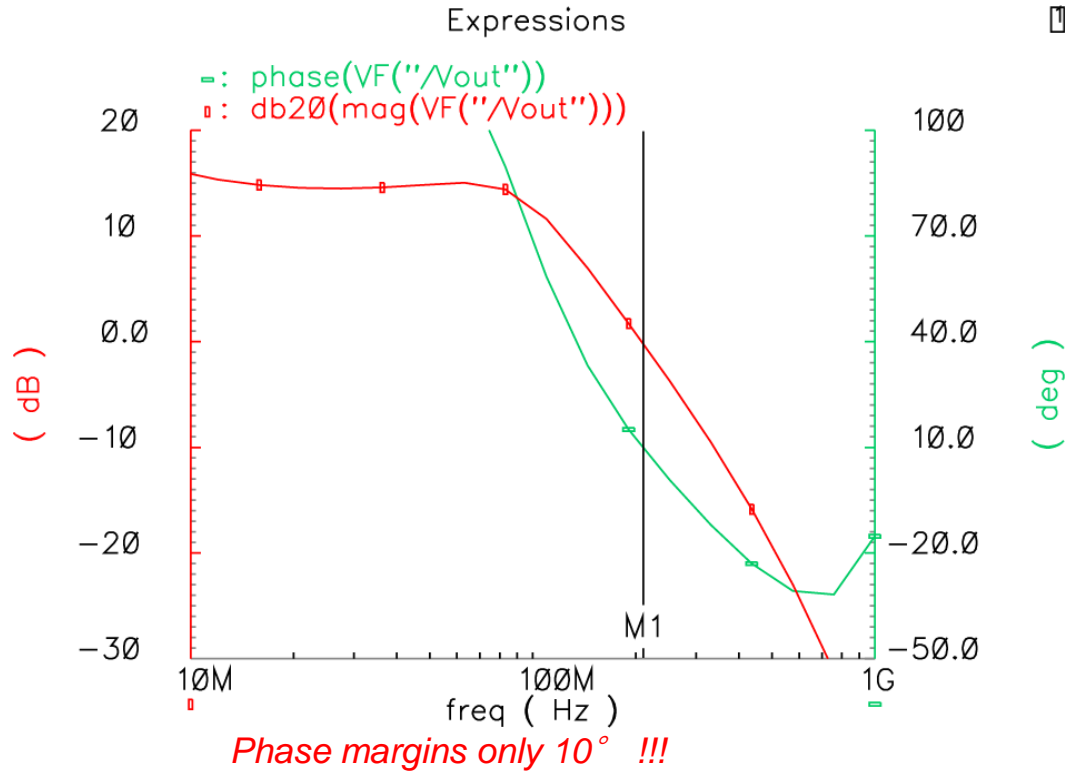

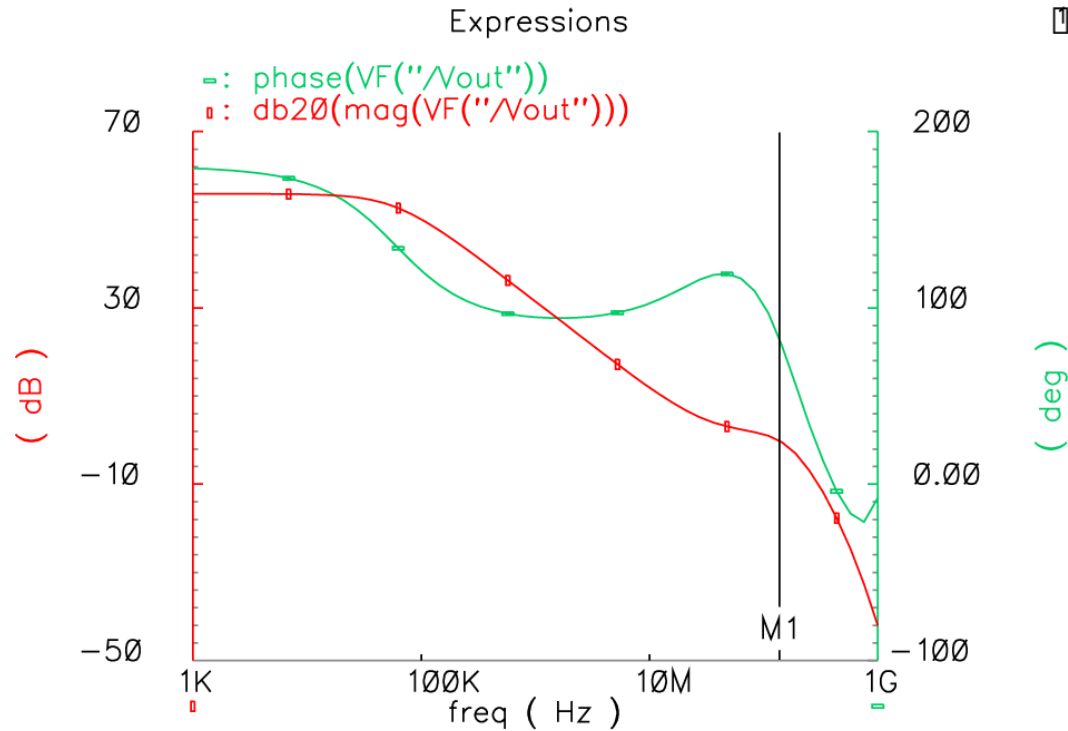- What to do?
 - Book: increase C_c
 - Try to decrease R_c



Give unit-gain freq of 133MHz with $PM=84^\circ$ with $R_c=2050\Omega$