



UiO : Department of Informatics
University of Oslo

IN5230
Electronic noise –
Estimates and countermeasures

Lecture 10 (Mot 7)
Modelling system noise



1

UiO : Department of Informatics
University of Oslo


- Modelling of noise must include:
 - Sensors
 - Bias and coupling network
 - Amplifiers
- We use our standard method:
 1. Determine the total noise at output: E_{no}
 2. Determine the system gain: K_t
 3. Divide E_{no} with K_t : $E_{ni}^2 = E_{no}^2 / K_t^2$

2

2


A general voltage noise model

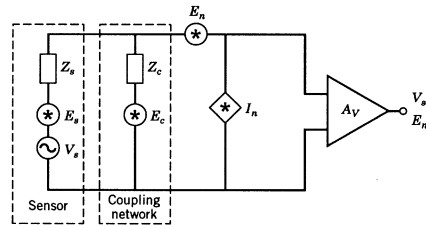- Equivalent noise voltage at the input – general expression:



$$E_{ni}^2 = A^2 E_S^2 + B^2 E_n^2 + C^2 I_n^2 Z_S^2 + D^2 E_C^2$$

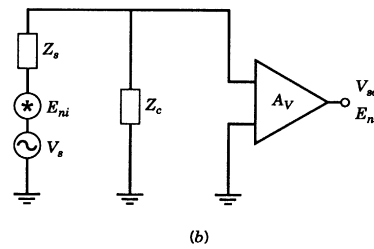- A, B, C and D are functions of resistors, capacitors, coils etc and not functions of currents or voltages.



3

A general current noise model

- Equivalent noise current at the input – general expression:

$$I_{ni}^2 = J^2 I_{ns}^2 + \frac{K^2 E_n^2}{Z_S^2} + L^2 I_n^2 + \frac{M^2 E_C^2}{Z_C^2}$$

- Neither J, K, L nor M are functions of voltage or current.
- It is irrelevant whether one calculates the equivalent input noise voltage or current.

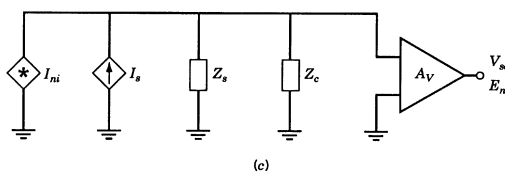


Figure 7-1 System noise model.

4

Effect of parallel load resistance 1/2


- Input (i.e. without R_p):

$$\frac{S}{N} = \frac{V_{so}^2}{E_{no}^2} = \frac{V_S^2}{E_S^2}$$

- Output (i.e. with R_p).

$$V_{so} = \frac{R_p}{R_S + R_p} V_S \quad E_{no}^2 = \left(\frac{R_p}{R_S + R_p} E_S \right)^2 + \left(\frac{R_S}{R_p + R_S} E_P \right)^2$$
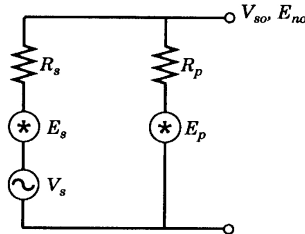
$$\frac{S_{ut}}{N_{ut}} = \frac{V_{so}^2}{E_{no}^2} = \frac{\left(\frac{R_p}{R_S + R_p} \right)^2 V_S^2}{\left(\frac{R_p}{R_S + R_p} \right)^2 E_S^2 + \left(\frac{R_S}{R_p + R_S} \right)^2 E_P^2} = \frac{V_S^2}{E_S^2 + \left(\frac{R_S}{R_p} \right)^2 E_P^2}$$



5

Effect of parallel load resistance 2/2

$$\frac{S_{ut}}{N_{ut}} = \frac{V_{so}^2}{E_{no}^2} = \frac{\left(\frac{R_p}{R_S + R_p} \right)^2 V_S^2}{\left(\frac{R_p}{R_S + R_p} \right)^2 E_S^2 + \left(\frac{R_S}{R_p + R_S} \right)^2 E_P^2} = \frac{V_S^2}{E_S^2 + \left(\frac{R_S}{R_p} \right)^2 E_P^2}$$

When $R_S = R_p$ then $E_S = E_P$ and we get that $(S/N)_{ut} = \frac{1}{2}(V_S^2/E_S^2) = \frac{1}{2}(S/N)_{inn}$. R_p equally reduces V_S and E_S but contribute in addition with its own noise. When $R_S \gg R_p$ decreases $(S/N)_{ut}$ towards zero, while when $R_S \ll R_p$ will $(S/N)_{ut}$ increase towards $(S/N)_{inn}$ which is the best that can be achieved.

6

6

Calculation with amplifier noise

1. Noise at output

$$E_{no}^2 = E_s^2 \left(\frac{R_p}{R_s + R_p} \right)^2 + E_n^2 + I_n^2 (R_p \parallel R_s)^2 + I_{np}^2 (R_p \parallel R_s)^2$$

2. System gain

$$K_t = \frac{R_p}{R_s + R_p}$$

3. Equivalent input noise

$$E_{ni}^2 = \frac{E_{no}^2}{K_t^2} = E_s^2 + \left(\frac{R_s + R_p}{R_p} \right)^2 E_n^2 + (I_n^2 + I_{np}^2) R_s^2$$

We compare with our well-known equation:

$$E_{ni}^2 = \frac{E_{no}^2}{K_t^2} = E_s^2 + E_n^2 + I_n^2 R_s^2$$

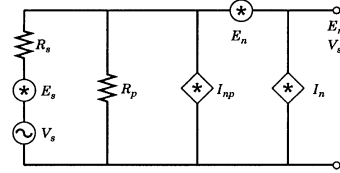


Figure 7-3 Amplifier and sensor models with shunt resistance.

- Terms in front of E_n : If $R_p \ll R_s$ we have that E_n will contribute a lot. If $R_s = R_p$ the contribution from E_n will be equal to $4E_n^2$. If $R_p \gg R_s$ contributes E_n with only E_n^2
- $I_{np}^2 R_s^2$ is a new term. This is the thermal noise in R_p .

7

Increased Rp & Vb

1)


R_p must be made as large as possible. If a certain voltage is required over R_s or a certain current through R_s we may change the bias voltage accordingly.

Example: $R_s = 1k\Omega$, $R_p = 1.5k\Omega$ and $V_B = 2.5V$. If we change to new values $R_p = 199k\Omega$ and $V_B = 200V$ the voltage over the sensor and the current through the sensor remains the same but the noise is significantly reduced.

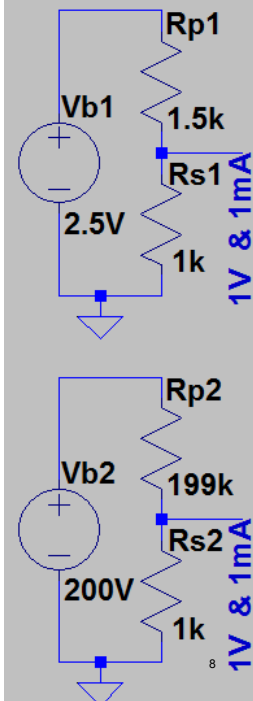
2)

Alternatively, maybe it is possible to use a coil instead of R_p ?


$$E_{ni}^2 = E_n^2 \left[\frac{R_s}{j\omega L} + 1 \right]^2 + I_n^2 R_s^2 + E_s^2$$



8

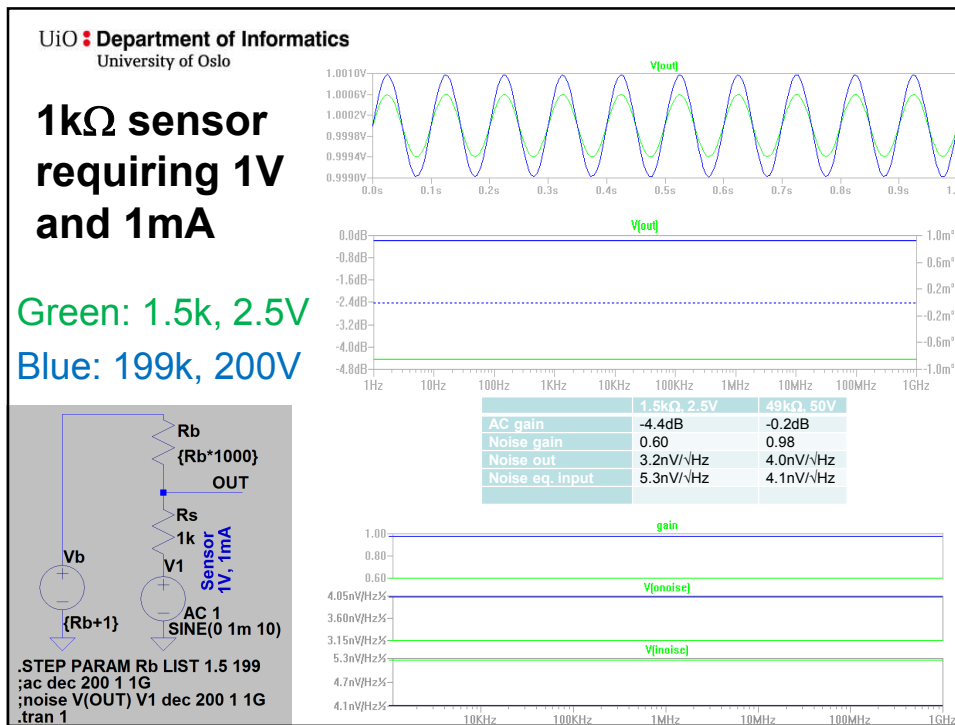


9

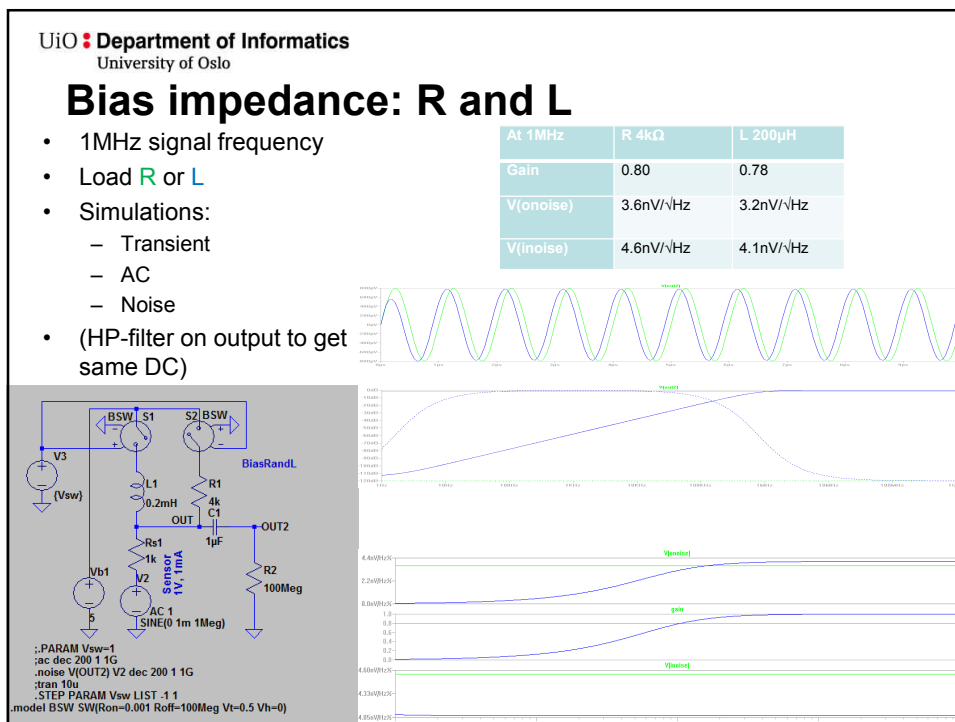

10

Effect of shunt capacitances

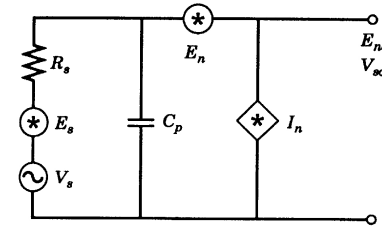Here we have replaced the resistance R_p with a capacitor C_p



$$1) \quad E_{no}^2 = E_s^2 \left(\frac{1}{R_s + \frac{1}{j\omega C_p}} \right)^2 + E_n^2 + I_n^2 \left(\frac{R_s \frac{1}{j\omega C_p}}{R_s + \frac{1}{j\omega C_p}} \right)^2 =$$

$$E_s^2 \left(\frac{1}{R_s^2 C_p^2 \omega^2 + 1} \right) + E_n^2 + I_n^2 \left(\frac{R_s^2}{R_s^2 C_p^2 \omega^2 + 1} \right)$$

$$2) \quad K_t^2 = \left(\frac{\frac{1}{j\omega C_p}}{R_s + \frac{1}{j\omega C_p}} \right) = \frac{1}{R_s^2 C_p^2 \omega^2 + 1}$$

11

11

$$3) \quad E_{ni}^2 = \frac{E_{no}^2}{K_t^2} = E_s^2 + E_n^2 (R_s^2 C_p^2 \omega^2 + 1) + I_n^2 R_s^2$$

We compare with our well-known expression:

$$E_{ni}^2 = \frac{E_{no}^2}{K_t^2} = E_s^2 + E_n^2 + I_n^2 R_s^2$$

$\Rightarrow E_n^2$ is multiplied by $(R_s^2 C_p^2 \omega^2 + 1)$. Note! $R_s^2 C_p^2 \omega^2$ will often be substantially less than 1.

Only the E_n^2 contribution increases.

NB! C_p is no noise source!

C_p is not the input capacitance of the amplifier. This is included in E_n , I_n and K_t .

12

12

Noise in a resonant circuit

1) Noise at output

$$E_{no}^2 = E_s^2 \left(\frac{X_{L_p} \parallel X_{C_p}}{R_s + X_{L_p} \parallel X_{C_p}} \right)^2 + E_n^2 + I_n^2 (R_s \parallel X_{L_p} \parallel X_{C_p})^2$$

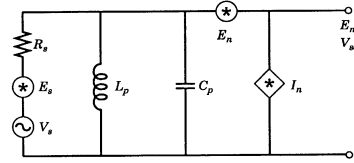


Figure 7-5 Resonant sensor equivalent circuit.

Calculation of parts:

$$\frac{X_{L_p} \parallel X_{C_p}}{R_s + X_{L_p} \parallel X_{C_p}} = \frac{1}{R_s \left(j\omega C_p + \frac{1}{j\omega L_p} \right) + 1} = \frac{1}{R_s \left(\frac{1 - \omega^2 C_p L_p}{j\omega L_p} \right) + 1} = \frac{j\omega L_p}{j\omega L_p + R_s - \omega^2 L_p C_p R_s}$$

$$R_s \parallel X_{L_p} \parallel X_{C_p} = \frac{1}{\frac{1}{R_s} + \frac{1}{j\omega L_p} + j\omega C_p} = \frac{j\omega R_s L_p}{j\omega L_p + R_s - \omega^2 R_s C_p L_p}$$

$$E_{no}^2 = E_s^2 \left(\frac{1}{R_s \left(j\omega C_p + \frac{1}{j\omega L_p} \right) + 1} \right)^2 + E_n^2 + I_n^2 \left(\frac{1}{\frac{1}{R_s} + \frac{1}{j\omega L_p} + j\omega C_p} \right)^2$$

13

13

2) Signal gain

$$K_i^2 = \left(\frac{X_{L_p} \parallel X_{C_p}}{R_s + X_{L_p} \parallel X_{C_p}} \right)^2 = \left(\frac{1}{R_s \left(jC_p \omega + \frac{1}{jL_p \omega} \right) + 1} \right)^2$$

3) Equivalent input noise

$$E_{ni}^2 = \frac{E_{no}^2}{K_i^2} = E_s^2 + E_n^2 \left| 1 + \frac{R_s (1 - \omega^2 C_p L_p)}{j\omega L_p} \right|^2 + I_n^2 \left(\frac{R_s \left(j\omega C_p + \frac{1}{j\omega L_p} \right) + 1}{\frac{1}{R_s} + \frac{1}{j\omega L_p} + j\omega C_p} \right)^2 = \text{well-known expression (without } C_p \text{ and } L_p \text{)}$$

$$E_s^2 + E_n^2 \left| 1 + \frac{R_s (1 - \omega^2 C_p L_p)}{j\omega L_p} \right|^2 + I_n^2 R_s^2$$

⇒ The I_n -coefficient is independent of frequency
 ⇒ The E_n -coefficient will have a weight larger than 1 except at resonance. At the resonance ($\omega^2 C_p L_p = 1$) is the reactance element 0 and the coefficient equal to 1. We will then end up with our well-known expression (without C_p and L_p).
 ⇒ L_p and C_p does not contribute itself but affects others.

14

14

The gain (top figure) is largest at resonance frequency. That is also the case for the noise output (in the middle). However, the equivalent noise at the input (bottom) is lowest at the resonance. This means that the signal is amplified more than the increase in noise at resonance.

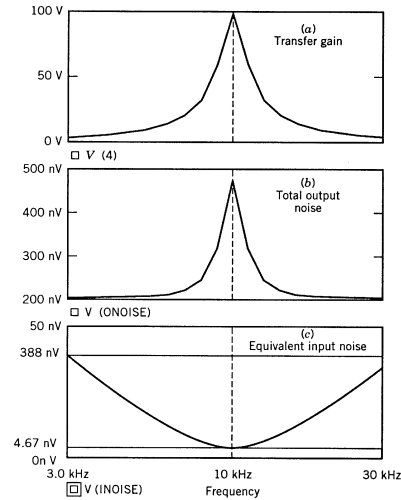


Figure 7-7 Plot of noise for RLC model.

15

15

Summary

- Resistance in parallel: $E_m^2 = E_s^2 + \left(\frac{R_s}{R_p} + 1\right)^2 E_n^2 + (I_n^2 + I_p^2) R_s^2$
- Capacitor in parallel: $E_m^2 = E_s^2 + (R_s^2 C_p^2 \omega^2 + 1) E_n^2 + I_n^2 R_s^2$
- Coil in parallel: $E_m^2 = E_s^2 + \left(\frac{R_s^2}{\omega^2 L^2} + 1\right) E_n^2 + I_n^2 R_s^2$
- Xs in signal path and Xp in parallel: $E_m^2 = E_s^2 + \left(\frac{R_s + X_s}{X_p} + 1\right)^2 E_n^2 + (R_s + X_s)^2 I_n^2$

Xs and Xp are combinations of capacitances and coils in series and/or parallel (No resistances!)


- XLC is a coil and a capacitor in parallel: $X_{LC} = \frac{j\omega L \cdot \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = \frac{j\omega L}{1 - \omega^2 LC}$

16

16


When we can not reduce the noise...

- Large SNR and DR is achieved either by reducing the noise or increasing the signal. Is it any potential for increasing the maximum signal range?
- Make the signal range approach the supply voltage range
 - The signal range in traditional amplifiers is only a limited region of the voltage supply region a)
 - Rail-to-rail amplifiers approach the full supply voltage range. However these amplifiers are much more complex. b)
- Use differential amplifiers
 - Differential amplifiers has twice the signal range (and better CMRR) but the component noise increases (from $\sqrt{2}$ and upwards).

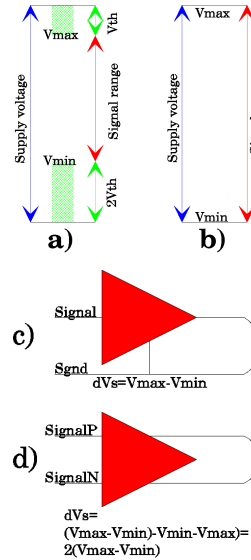


17

Rail-to-rail diff in/out amplifier

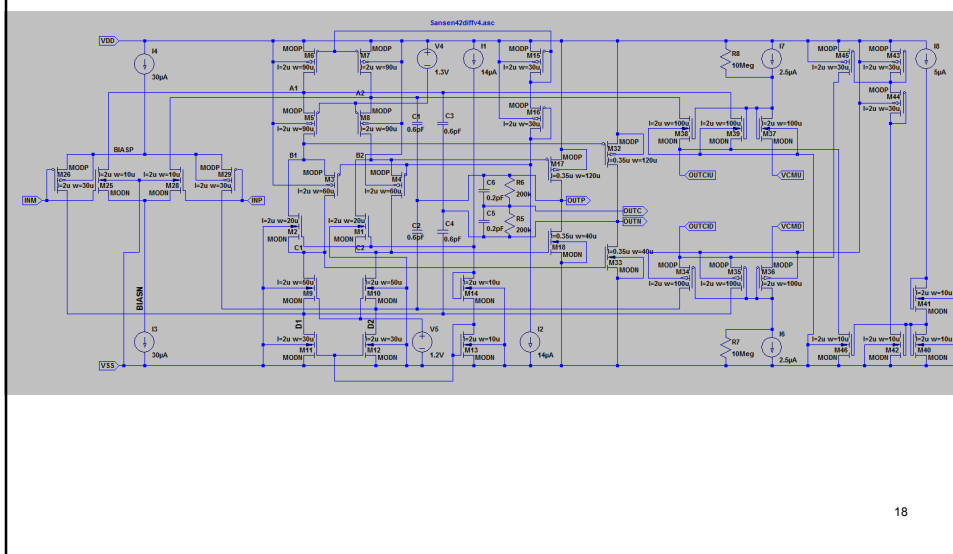

18

Rail-to-rail test bench

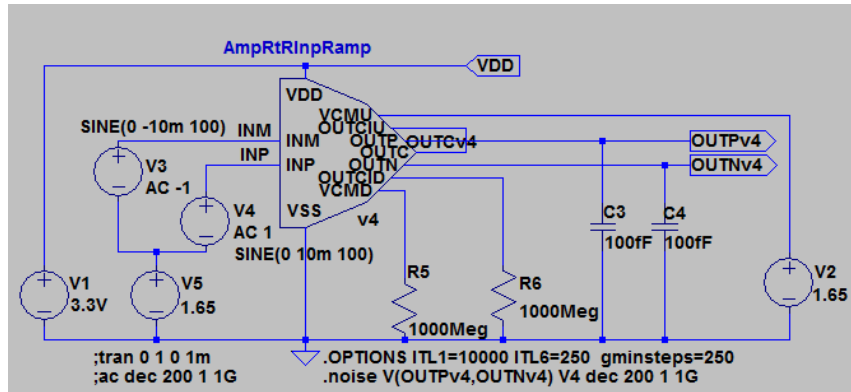


19

19

Rail-to-rail amplifier

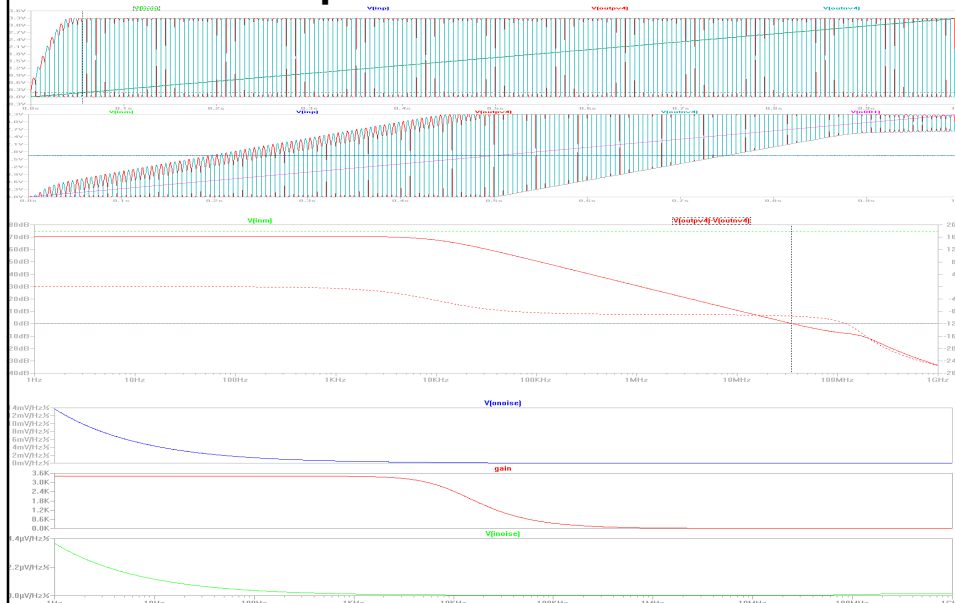- $V_{out_cm}=1.65V$, $V_{in_cm}=0-3.3V$
- $V_{in_cm}=1.65V$, $V_{out_cm}=0-3.3V$
- AC ($V_{out_cm}=V_{in_cm}=1.65V$)
- Noise ($V_{out_cm}=V_{in_cm}=1.65V$)



20

UiO Department of Informatics
University of Oslo

NCM-eye

- Goal: Measure resistance in rock
- Two ASICs designed for 200° C operation temperature
- Measurement setup:
 - 100-200V AC is set up over the rock region to be inspected
 - Sensor front ends with very high input impedance (10-100GΩ) measure the local voltage level
 - Voltage differences between neighbour pairs are found
 - Resulting values are converted into a digital format and feed into common buses

21

UiO Department of Informatics
University of Oslo

Very high input impedance preamp

- GBW=10MHz
- $Z_{in} = 1-100G\Omega$

22

Active shield

- Names: Active shield/Driven guard/bootstrapping
- “Makes invisible”
- Purpose:
 - Achieve extremely high input impedance
 - Isolate from noise sources
 - Eliminate parasitic capacitive loads at input

INS230


New foils

23

23

2.2x Active shield - theory

- The effective capacitance experienced by a signal depends on the signal on the other side of the capacitor.
- If the other side is grounded the effective capacitance will be the “basic” capacitance. If it is in opposite phase it will be larger while it will be less if it is in phase. If the signal is equal, the capacitance will disappear.

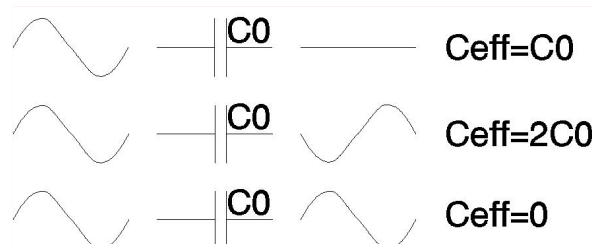

INS230

New foils

24

24

Effective capacitance

C_u : Unity capacitance (when $V_m=0$)

V_s : (AC) signal voltage

V_m : (AC) voltage on opposite side of C

For simplicity we consider only in phase (0°) or in opposite phase (180°) with a gain $|m|$. $V_m = mV_s$ where $m \in R$


The change in charge on both capacitors are dQ .

$$dQ = C_u dV = C_u (V_m - V_s)$$

The S node experience this charge change over V_s which represents an effective capacitance C_{eff} .

$$C_{eff} = \frac{dQ}{dV} = \frac{Q}{V_s} = \frac{V_m - V_s}{V_s} C_u = \frac{m - 1}{1} C_u$$

$$C_{eff} = |m - 1| C_u$$

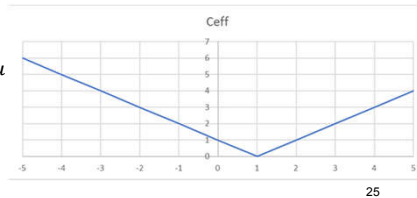


IN5230

New foils


25

25

2.2x Active shield


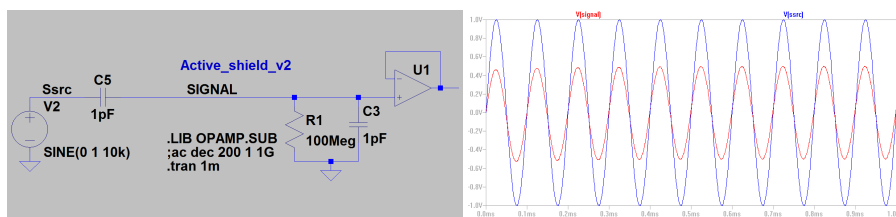


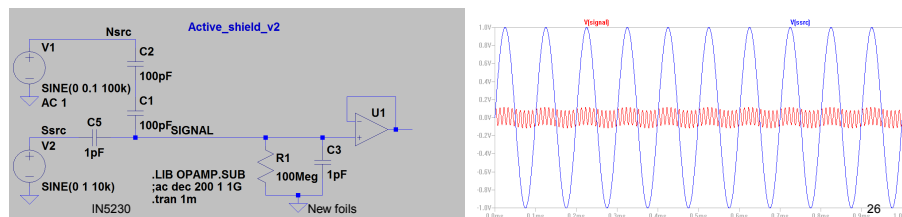- Above: What we want
- Below: What we have





26

2.2x Active shield

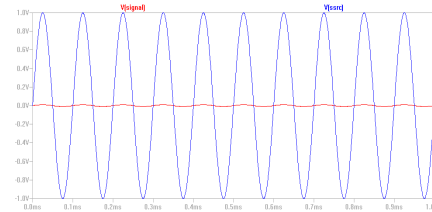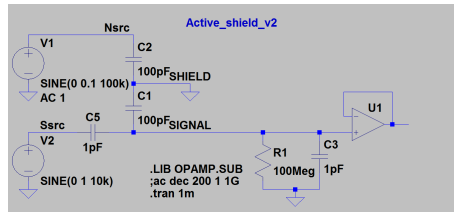

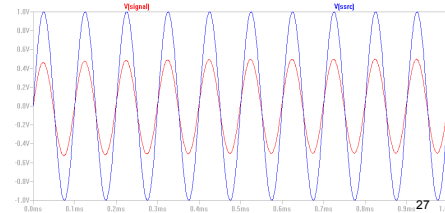
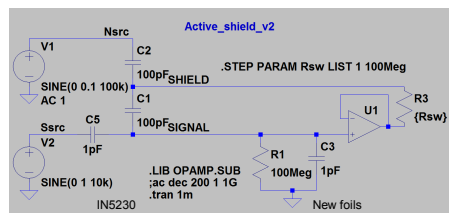
- Above: Grounded screen
- Below: Active screen




27

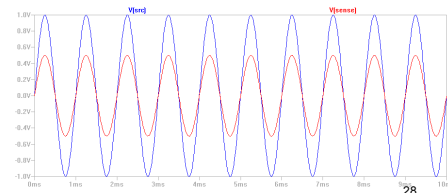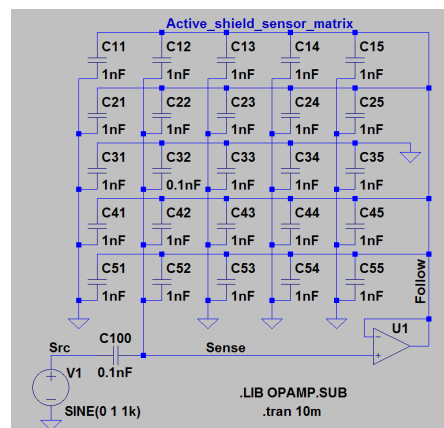2.2x Active shield – Sensor matrix example


- Active shield can be used to select one capacitor in a sensor matrix.
- Our example target is C32
- Method: Ground the C32 row and connect all other rows to active shield.
- The other columns are grounded but may be connected to active shield to reduce power.
- Simulation shows $V(\text{Sense})=V(\text{Src})/2!$ Thus only C100 and C32 influence and we have succeeded!



28

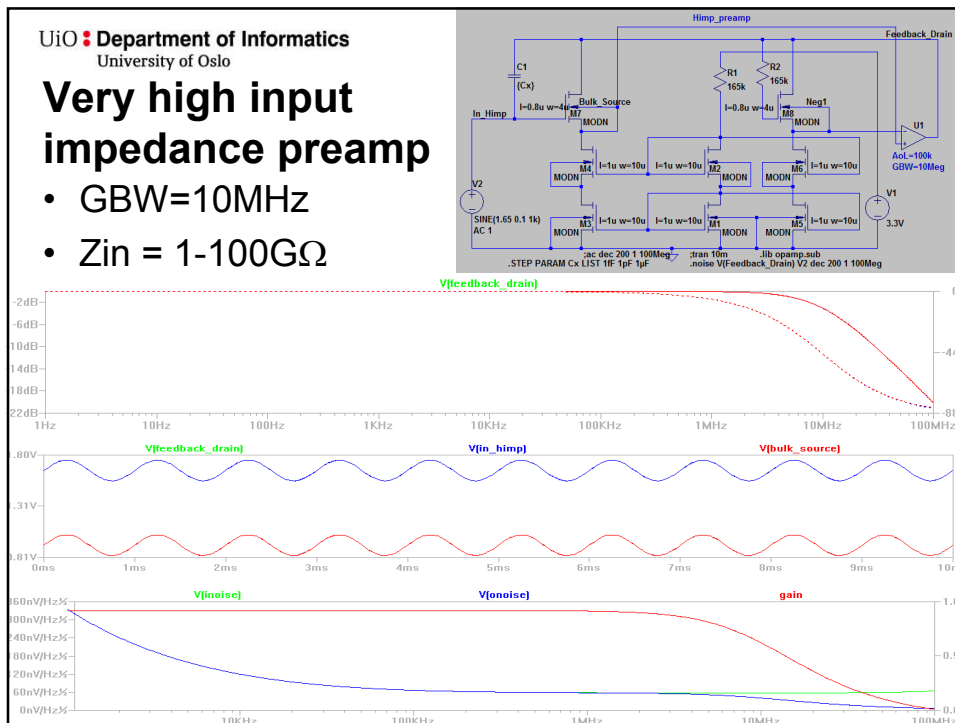

29

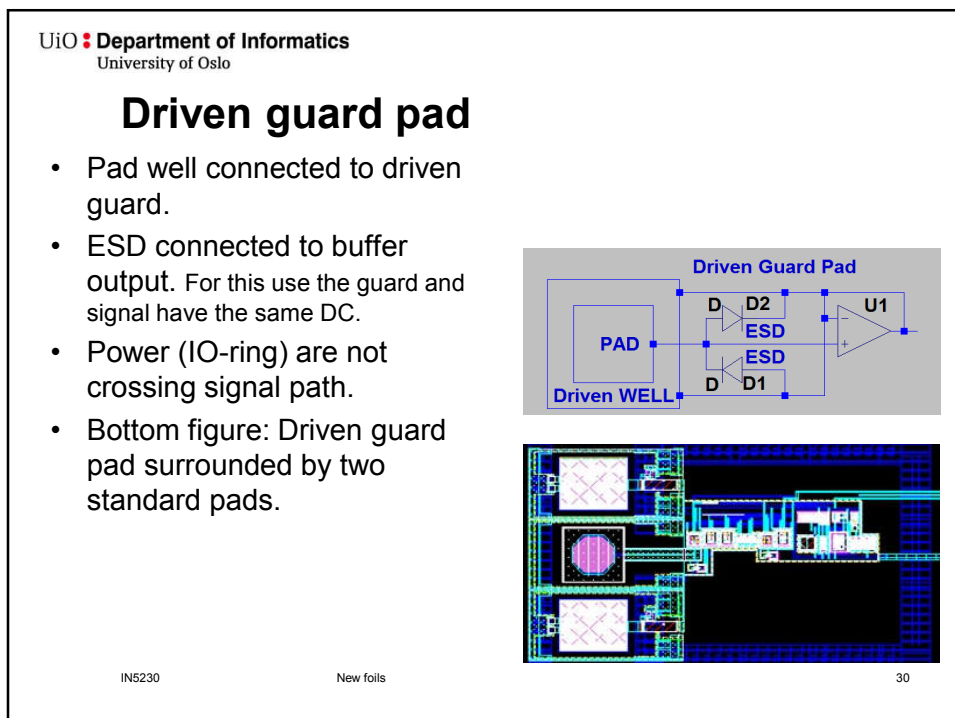

30