



UiO : Department of Informatics
University of Oslo

IN5230
Electronic noise –
Estimates and countermeasures

Mandatory lab 3 LTspice circuit simulations



1

UiO : Department of Informatics
University of Oslo

Mandatory lab

Send report by email to joar@ifi.uio.no and
jonheri@ifi.uio.no.

Deadlines:

- Schematic – subtask 2: 08:00 Monday 11th of November
- Final Report –08:00 Friday 22th of November,

Assessment: Approved / Not approved.

Reports are submitted on an individual basis. The tasks will consist of schematics that are used, simulation results, text EXPLAINING what has been done as well as an analysis of the results. Put up a summary table and comment at the end of each task when relevant. USE WHITE/LIGHT BACKGROUND for the plots! Avoid yellow curves.

2

2

Mandatory 3

- You are going to be using LTspice
- In the specific, you are going to run NOISE simulations within LTspice



3

3

Simulation modes


	Time	Frequency
Signal (standard)	.TRAN	.AC
Component noise	.TRAN V (added by user: standard sources or from file) .NOISETRAN (noise sources generated by software)	.NOISE (noise sources generated by software)
Coupling noise	.TRAN --- V (manually added by user: standard V-sources or from file) --- R, C or L modelling parasitic (Extracted by software or manually added by user)	.AC --- V (manually added by user: AC) --- R, C or L modelling parasitic (Extracted by software or manually added by user)



4

4


Transient component noise simulation

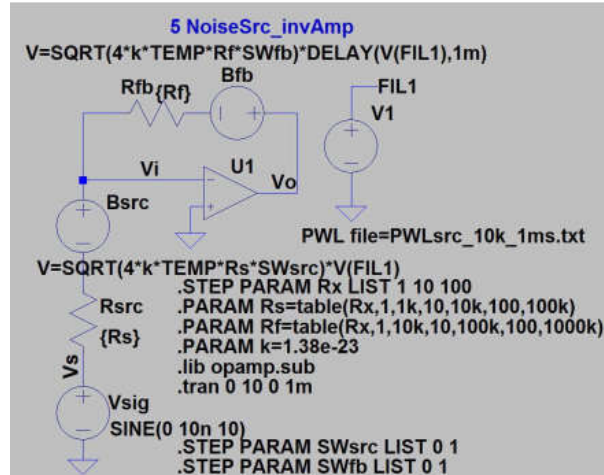

5

5

Transient component noise simulation

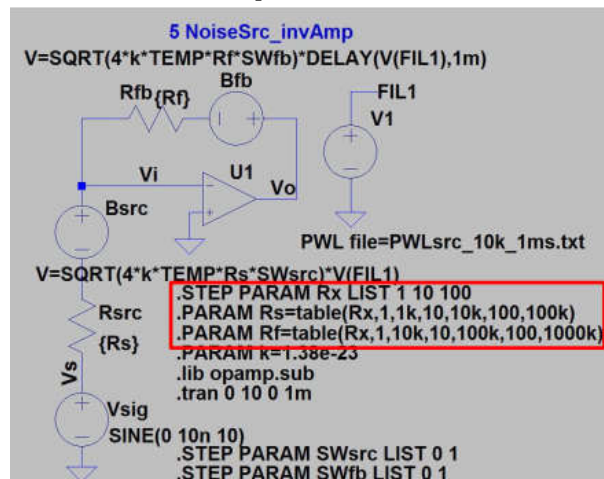

6

6

Preparing CMOS model for manatory 3

Will use transistor models for an integrated circuit: 0.35m CMOS from AMS (Austria Micro Systems)

Preparation

1. Include transistor model card
2. Include symbols
3. Set correct model for transistors in schematic
4. Set correct length and width for transistors in schematic

7

7

Preparing CMOS model for manatory 3

1. Generally transistor models can be included as:
 - A model in the standard library file,
 - As a private library file. Must include link in schematic, or
 - As «text» in the schematic

⇒ We chose the first alternative and replace <program files>/LTC/LTspiveIV/lib/cmp/standard.mos with our own file
2. Transistor symbols
 - We use our own transistor symbols (that show widths, lengths etc.). They must be on the same directory as we have our schematics (nmos.asy, pmos.asy)

8

8

Preparing CMOS model for manatory 3

3. Correct transistor model:
 - Change the transistor model name for NMOS transistors to MODN and for PMOS to MODP
4. Change transistor width and length
 - Set the correct transistor sizes in each transistor. In figures the transistor sizes are often given in Width/Length. Remember to add «u» or «μ» after the numbers to give correct value. If not the sizes will be interpreted as meters (with no warning). Right click on the component to change height and width.

9

9

LTspice: .NOISE analysis

.NOISE is used to simulate component noise in the frequency-domain. The simulator includes by itself noise for all components in the schematic.

Example: **.NOISE V(out) V1 dec 200 1m 1G**

- Out: Name of network node
- V1: Name of source. May be voltage or current
- Dec: Type of sweep (decad, octave, linear or list)
- 200: Number of points per decade/octave
- 1m: Start frequency (1m = 1 milli Hz, 1Meg = 1 Mega Hz)
- 1G: Stop frequency

10

10

LTspice: .MEAS – measure and save

.MEAS directive is used to measure and save some variables in the spice «error log» (right click →View→Spice Error Log)


Examples (AC – for AC simulation – NOISE for noise simulation):

- **.MEAS** AC Smax MAX MAG(V(out))
- **.MEAS** AC Bw TARG MAG(V(out)) VAL=Smax/SQRT(2) FALL=1
- **.MEAS** AC GBW WHEN MAG(V(out))=MAG(V(in))
- **.MEAS** NOISE N_R1 FIND V(r1) AT 10k
- **.MEAS** NOISE Ni10k100k INTEG V(inoise) TRIG AT=1k TARG AT=100k

11

11

2014-3-2-amp8t_10_10_noise_invert.asc

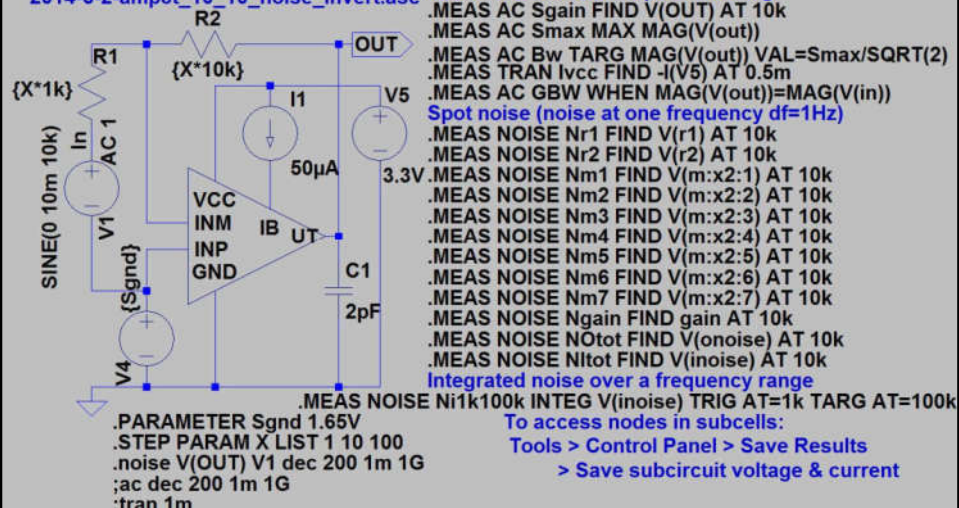


12

12

Inverter transistor example

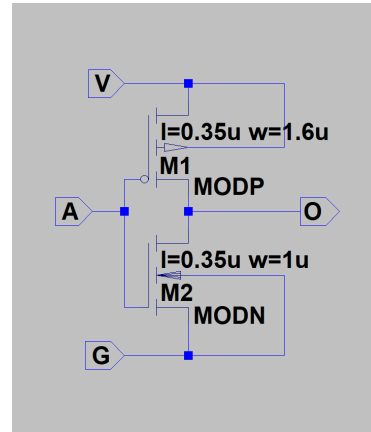
- PMOS: Outgoing arrow connected to high supply
- NMOS: Incoming arrow connected to low potential



13

13

1. Ideal amplifier

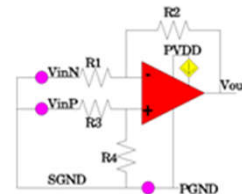

We will first look at an ideal amplifier in an ideal differential amplifier configuration. You can copy the amplifier symbol from the "opamp" circuit in the "Educational" area. Let the opamp Aol be 100k and the GBW be 10Meg. Be sure to get the "include" statement. Build a resistive network around as indicated in Figure 3-4 "Differential amplifier using one op amp" page 56 (figure in Motchenbacher). For all cases the relation between the resistors will be $R1=R3=R_x$ and $R2=R4=10R_x$.

a) Let R_x be 1k Ω , 10k Ω and 100k Ω . Is the gain different in the three cases?

Run .NOISE simulations and find the output noise and equivalent input noise for the three cases at 10kHz. Find the total equivalent input noise both at the positive and the negative input by simulation (in the region where the gain is larger than one). What type of noise is present here?


b) Calculate manually the noise for each of the resistor elements i) locally (at their position), their value at the ii) output and their equivalent value at the iii) input. Use the table below. Which of them has the largest contribution at the output and at the input? Which of these three can you find in the simulation results?

Example	Local noise (nV/ $\sqrt{\text{Hz}}$)	Gain to output	Noise at output (nV/ $\sqrt{\text{Hz}}$)	Equivalent noise at input (nV/ $\sqrt{\text{Hz}}$)
R1				
R2				
R3				
R4				
Total				

14

14


2. Simple CMOS amplifier

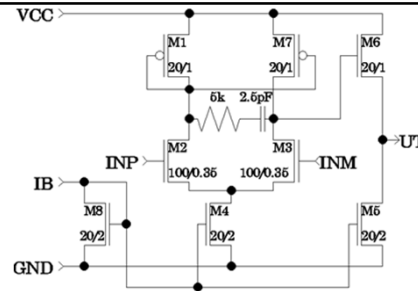

- Perform AC analysis for the amplifier without feedback (i.e. open-loop). Let the common mode voltage (i.e. DC voltage of input signal) be 1.65V. Do AC analysis with a signal on the positive input (ACpos=1, ACneg=0), on the negative input (ACpos=0, ACneg=-1) and with differential signals on both inputs (ACpos=1, ACneg=-1).
- Replace the ideal amplifier in the feedback network in task "1 Ideal amplifier" with our new amplifier. Let $R_x = 1\text{k}\Omega$. Inspect the simulation results on the positive input and the output. What is the frequency range at which the flicker noise is dominant?
- We would like to know the (spot) noise at some frequencies and the integrated noise over some frequency ranges. Find the (positive) input and output noise at 1Hz, 1kHz, 1MHz and 1GHz. Then find the noise for the areas 1Hz-1kHz, 1kHz-1MHz and 1Hz-1MHz. (Use the .MEAS statement). How can we manually calculate the noise in the range 1Hz-1MHz from the two subareas we found through simulation?
- Perform the same NOISE simulation as in task 1 with $R_x = 1\text{k}\Omega$, $R_x = 10\text{k}\Omega$ and $R_x = 100\text{k}\Omega$. Simulate with a capacitive load of 1pF. List the six largest sources of noise at 1MHz_{T5} for all three cases. Comment on the result.

15

3. Open loop, 10x gain and closed loop

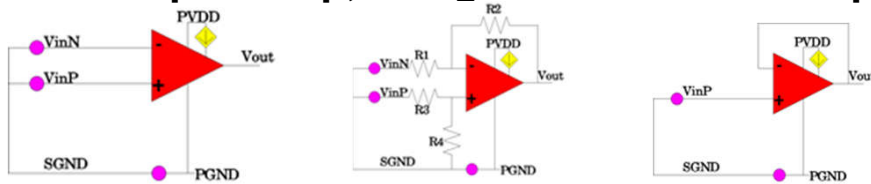


In this task you shall find the spot noise at 1MHz and the integrated noise from 1 Hz to 1 MHz at output and the positive equivalent input. Find this for open loop, for 10x (with the network over) as well as a follower. Present your results in a table.

The small pink circles are voltage sources. The voltage sources between SGND and PGND is a 1.65V DC source.

16

16

4. Common source input stage - RF

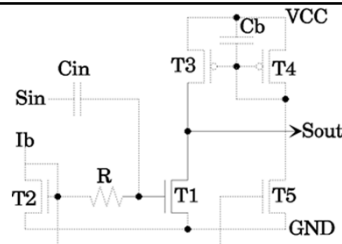

a) How large must C_{in} be to not mute the signal more than about 10%? Generate a figure with C_{in} on the x-axis and signal strength on the Y-axis.

b) How large must R be to not contribute significantly (<10%) of the total noise? (R will have minimum contribution for small and large resistor values. However, at small R values the resistor will mute the input resulting in a low gain. Hence, we have to go for a sufficient large resistor value.)

(You may use `.MEAS NOISE N_r1_onoise FIND V(r1)/V(onoise) AT 1Meg` to find the relation between R_1 noise and total noise.)

c) What does the C_b do? How much noise reduction can we achieve with C_b and how large must C_b be to achieve this? What is the gain, noise on the output and equivalent input noise now with a large C_b ?

Use the values you have found for C_{in} , R and C_b in the following.


d) Try doubling the width of the NMOS transistor, the length of the NMOS transistor, the PMOS transistor width and length of the PMOS transistor. Find the output noise, equivalent input noise as well as the gain for these 5 setups (reference + 4 variations) at 1MHz and put them up in a table.

e) Increase the power I_b in steps of $10\mu A$ from $10\mu A$ to $100\mu A$, and find the output noise, equivalent input noise and gain at 1MHz. Plot the equivalent input noise as a function of current.

f) Make copies of the present structure and replace MODN and MODP (3.3V models) with the standard LTspice NPN and PNP transistors. Put up a table with the output noise, equivalent input noise and gain for the two¹⁷ cases and comment on your results.

17

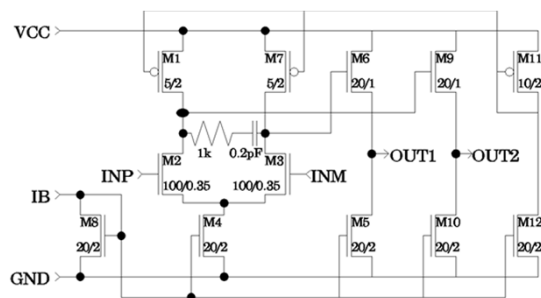5. CMOS amplifier with differential input and output



Use the same input forces and the same transistor models as in the previous task.

a) Find the gain for each signal input, the differential gain, output noise and equivalent input noise with a $50\mu A$ current bias.

b) Set up a simulation to find the effects of noise from the supply voltage V_{CC} . Find impact on each of the outputs individually and on the difference between the outputs. Do the same simulation first where M_2 and M_3 are identical (as defined above) and then with the width of the M_2 1% greater than the width of M_3 . Put the results in a table and comment.

d) Try to specify the variation in power consumption at V_{CC} when the input signal is a 1MHz sine with amplitude 10mV.

18