



Boolsk algebra

tirsdag 24. januar 2017 10.07

$$3 \text{ input} = 2^3 = 8$$


010100

-  AND \cdot $x \cdot y$
-  OR $+$ $x + y$
-  NOT $'$ \bar{x} x'

	X	Y	AND	OR
0	0	0	0	0
1	0	1	0	1
2	1	0	0	1
3	1	1	1	1

X	NOT
0	1
1	0

$$F = ab + a'b \Rightarrow b(a+a')$$

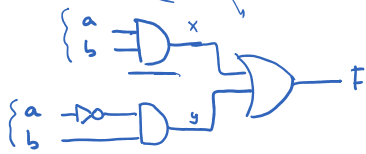

a	b	x	y	F
0	0	0	0	0
0	1	0	1	1
1	0	0	0	0
1	1	1	0	1



a	\bar{a}	OR
0	1	1
1	0	1

$$b \cdot 1 = b$$

b	1
0	1
1	1

DeMorgans theorem

$$(x \cdot y)' = x' + y'$$

$$(x + y)' = x' \cdot y'$$

$$\overline{\overline{xy}} = xy$$

$$F = x'y'z + x'yz + xy'$$

sum av produkt

$$F = x'z(y' + y) + xy'$$

$$F = x'z(1) + xy'$$

$$F = x'z + xy'$$

$$F = \sum(0, 1, 2, 5, \dots)$$

$$F = S(\dots)$$

Produkt-av-sum

$$F = (a+b+c)(a+b+c')(\dots)$$

$$(x+y)' = x' \cdot y'$$


$$F = \prod(0, 1, \dots)$$

Min terms

	a	b	c	F
m ₀	0	0	0	0
m ₁	0	0	1	1
m ₂	0	1	0	1
m ₃	0	1	1	0
m ₄	1	0	0	1
m ₅	1	0	1	1
m ₆	1	1	0	0
m ₇	1	1	1	0

$$F = \sum(1, 2, 4, 5, 6)$$
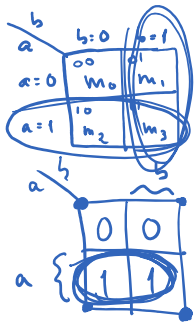
$$F = a'b'c + a'bc' + a'b'c' + ab'c + abc'$$



a b	F
00	0
01	0
10	1
11	1


$$f = ab' + ab = a(b' + b) = a \cdot 1 = a$$

$$F = a$$

$$F = a$$

a	bc	00	01	11	10
0	m ₀	m ₁	m ₃	m ₂	
1	m ₄	m ₅	m ₇	m ₆	

a b c	0	1
00	m ₀	m ₁
01	m ₂	m ₃
11	m ₆	m ₇
10	m ₄	m ₅

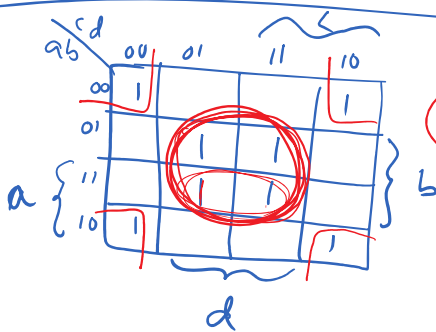

$$F = \underline{bd} + \underline{b'd'}$$


$$F = b \odot d$$

b d	F
00	1
01	0
10	0
11	1

XOR




a b c	xor
000	0
001	1
010	1
011	0
100	1
101	0
110	0
111	1

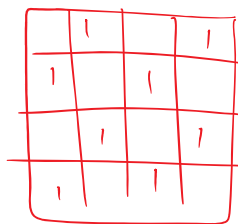


XNOR



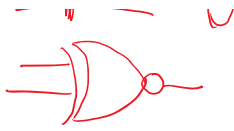


a	b	NAND
0	0	1
0	1	1
1	0	1
1	1	0

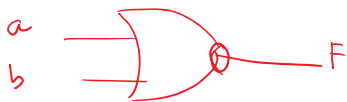



NOR

a	b	NOR
0	0	1
0	1	0
1	0	0
1	1	0

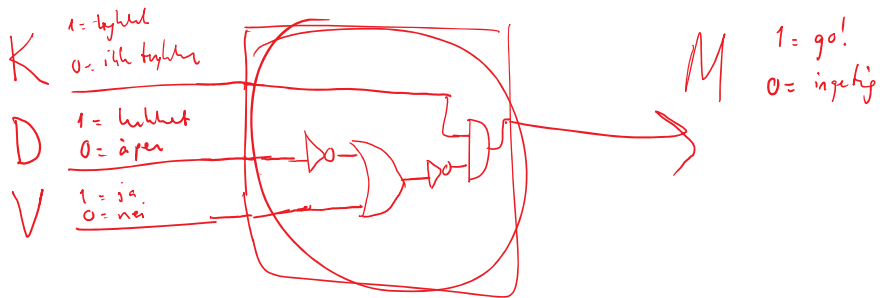

KVD	M
000	0
001	0
010	0
011	0
100	0
→ 101	1
110	0
111	0


KV'D

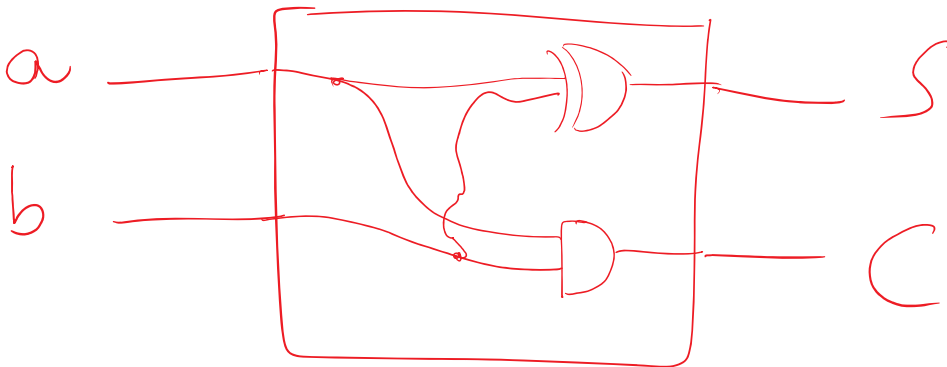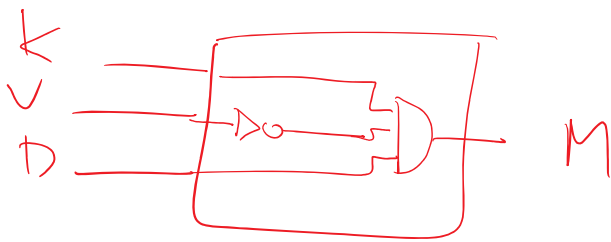

a	b	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

~~For~~
 $r = a \oplus b$.. - 1



$$s = a'b + ab' = a \oplus b$$

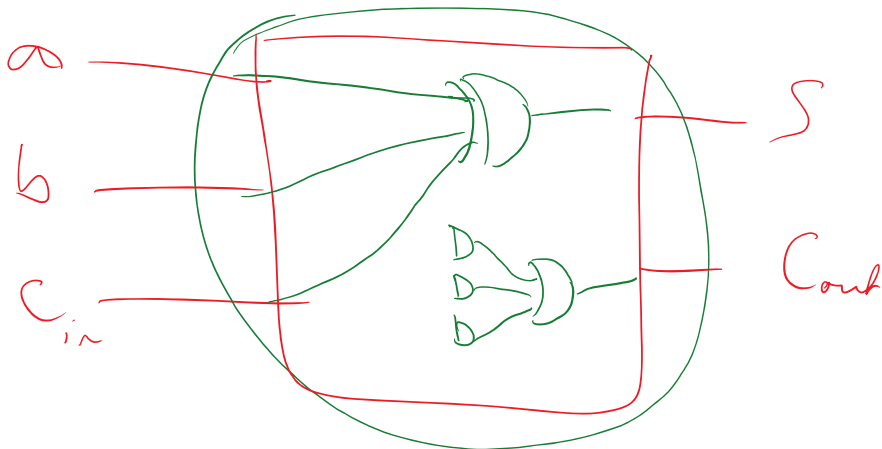

a	b	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = a \oplus b \oplus c$$

$$C_{out} =$$

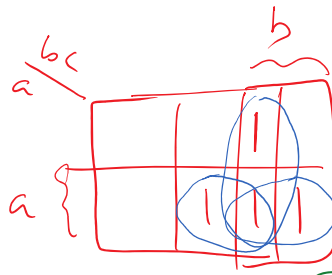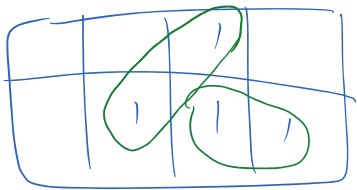

$$C_{out} = ac + bc + ab$$

