

# INF2270, exercise on combinational logic

Omid Mirmotahari

January 22, 2012

## **Abstract**

In these exercises you can test your skills in simplifying combinational logic using the tools of Boolean logic, truth tables and Karnaugh maps.

## **Exercise 1:**

- (a) Analyse the combinational logic circuits in figure 1 and write down the corresponding Boolean function!
- (b) Write down the functions as truth tables!
- (c) Use the tables to write Karnaugh maps!
- (d) Use the Karnaugh maps to derive minimal 'sum of products' Boolean functions!
- (e) Draw the resulting combinational logic circuit!

Note that the resulting circuit might not always have a smaller gate count, but it will always be a standard format with only ANDs and ORs, which can be an advantage for implementation too.

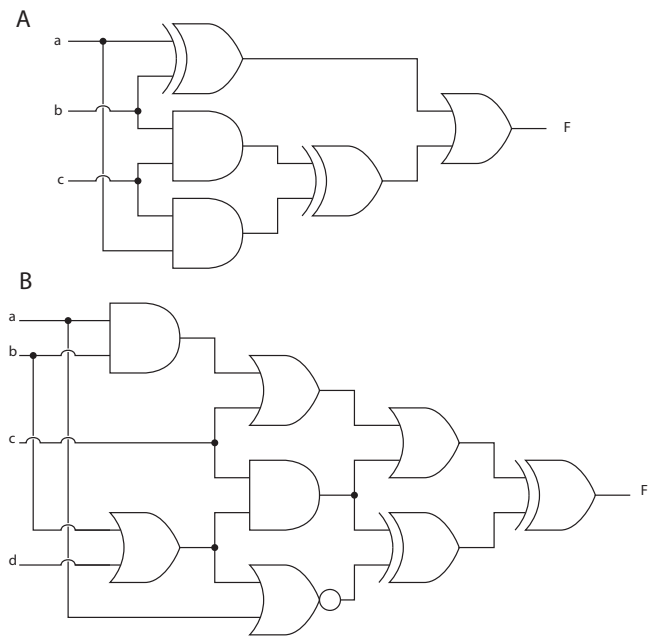


Figure 1: Two examples of (overly complicated) combinational circuits

## Exercise 2: Adder

- (a) Construct a one-bit adder. Draw the truthtable, simplify if possible using Karnaughmap and draw the circuit.
- (b) Construct a two-bit adder.

## Exercise 3: Gates

- (a) List the truthtable for a 3-input AND-, OR-, NOR-, NAND- and XOR-gates.
- (b) Demonstrate how to build 3-input AND-, OR-, NOR-, NAND- and XOR gates with just using 2-input gates.

## Exercise 4: Simplify Expressions

Simplify the following Boolean expressions to a minimum number of literals:

- (a)  $xy + xy'$
- (b)  $(x+y)(x+y')$
- (c)  $xyz + x'y + xyz'$
- (d)  $(A+B)'(A'+B)'$
- (e)  $ABC + A'B + ABC'$
- (f)  $x'yz + xz$
- (g)  $(x+y)'(x'+y')$
- (h)  $xy + x(wz + wz')$
- (i)  $(BC' + A'D)(AB'+CD')$

Reduce the following Boolean expressions to the indicated number of literals:

- (a)  $A'C' + ABC + AC'$  *to three literals*
- (b)  $(x'y' + z)' + z + xy + wz$  *to three literals*
- (c)  $A'B(D'+C'D) + B(A+A'CD)$  *to one literal*
- (d)  $(A'+C)(A'+C')(A+B+C'D)$  *to four literals*

Find the complement of  $F = x+yz$  then show that  $FF'=0$  and  $F+F' = 1$ .

List the truthtable for the function:  $F = xy + xy' + y'z$

Good Luck :)