

INF3410/4411, Fall 2018

Philipp Häfliger
hafliger@ifi.uio.no

Excerpt of Sedra/Smith Chapter 10: Feedback

Content

General Feedback Structure (book 10.1)


Effect on Poles and Stability (book 10.8, 10.9)

Content

General Feedback Structure (book 10.1)

Effect on Poles and Stability (book 10.8, 10.9)

General Concept

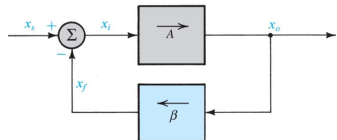

$$A_f = \frac{A}{1 + A\beta}$$
$$\approx \frac{1}{\beta} \text{ for } A\beta \gg 1$$

A_f : closed loop gain

$A\beta$: loop gain


β normally considered to be free of any frequency dependency!)

Content

General Feedback Structure (book 10.1)

Effect on Poles and Stability (book 10.8, 10.9)

A Has a Single Pole

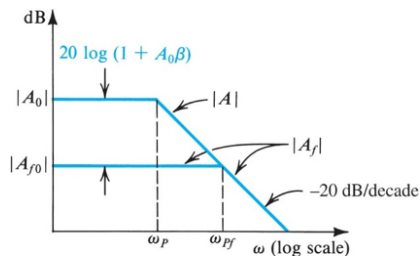

(b)

$$A_f = \frac{A_0}{1 + A_0\beta}$$
$$\omega_{pf} = \omega_p(1 + A_0\beta)$$


A Has Two Real Poles

Solving for poles: $1 + A(s)\beta = 0 \Rightarrow$

$$s = -\frac{1}{2}(\omega_{p1} + \omega_{p1}) \pm \frac{1}{2}\sqrt{(\omega_{p1} + \omega_{p1})^2 - 4(1 + A_0\beta)\omega_{p1}\omega_{p1}}$$
$$Q = \frac{\sqrt{(1 + A_0\beta)\omega_{p1}\omega_{p1}}}{\omega_{p1} + \omega_{p1}}$$

Generally more separation between ω_{p1} and ω_{p1} (i.e. a dominant pole) helps to keep A_f stable at higher loop gains.

Why the Resonance?

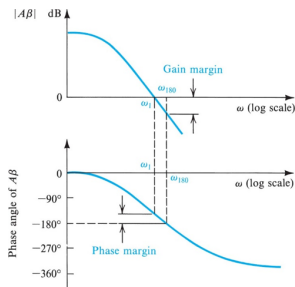

Negative feedback should not lead to amplification. The crux: a phase shift $\phi = -180^\circ$ turns negative feedback into positive feedback. If the loop gain $A\beta > 1$ at such a point, the circuit has infinite gain, i.e. is unstable.

In a low pass circuit the difference of the phase from -180° , i.e. $\phi + 180^\circ$ where the loop gain becomes unity ($A\beta = 1$ or $A = \frac{1}{\beta}$) is the *phase margin* (PM). A high PM indicates no or little resonance. A negative phase margin indicates an unstable circuit.