

INF3410/4411, Fall 2018

Philipp Häfliger
hafliger@ifi.uio.no

Excerpt of Sedra/Smith Chapter 2: Basic Circuits with OpAmps

Content

The Ideal Opamp (book: 2.1)

Some Circuits with OpAmps (book:2.2-2.5)

DC Imperfections (book:2.6)

Closed Loop Frequency Response (book:2.7)

Large Signal (Non-Linear) Effects (book:2.8)

Content

The Ideal Opamp (book: 2.1)


Some Circuits with OpAmps (book:2.2-2.5)

DC Imperfections (book:2.6)


Closed Loop Frequency Response (book:2.7)

Large Signal (Non-Linear) Effects (book:2.8)


Circuit Symbol

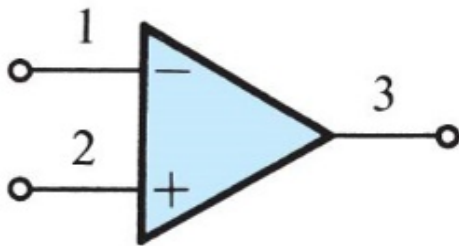

Circuit Symbol with Supplies

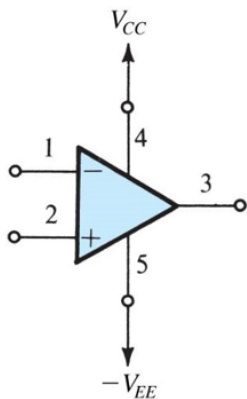


(a)

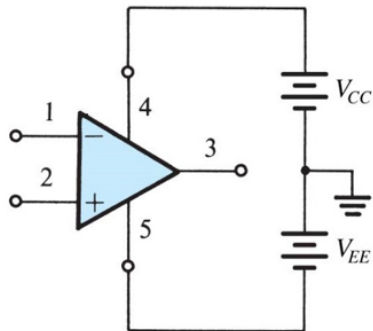


(b)

Ideal Operational Amplifier

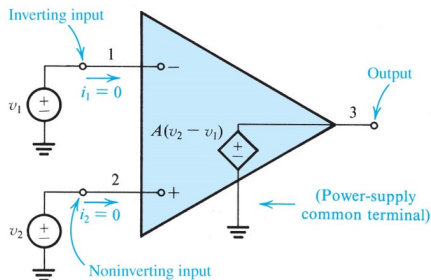

The *ideal* operational amplifier: Voltage mode (infinite input resistance/impedance, zero output resistance/impedance), single-ended-output, differential-input, zero common-mode gain, infinite open loop gain, infinite bandwidth.

Differential- and Common-Mode Input

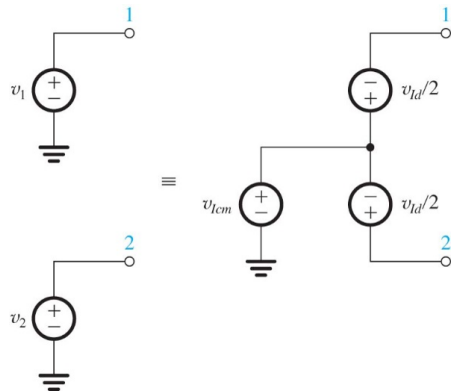

$$v_{Id} = v_2 - v_1 \quad (2.1)$$

$$v_{Icm} = \frac{v_2 + v_1}{2} \quad (2.2)$$

Content

The Ideal Opamp (book: 2.1)


Some Circuits with OpAmps (book:2.2-2.5)

DC Imperfections (book:2.6)

Closed Loop Frequency Response (book:2.7)


Large Signal (Non-Linear) Effects (book:2.8)

Basic Inverting Amplifier

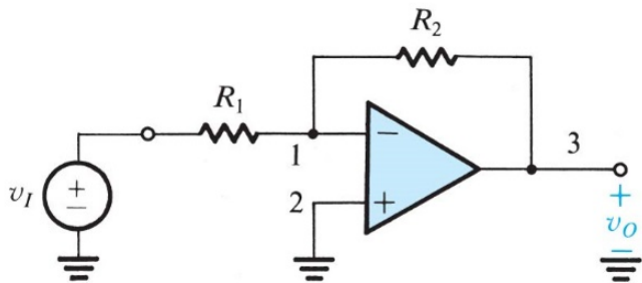

$$\frac{v_O}{v_I} = -\frac{R_2}{R_1} \quad (\text{page 101})$$


Basic Inverting Amplifier Analysis

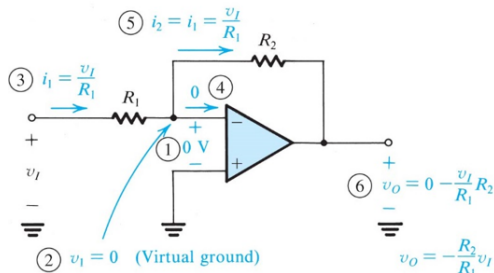

(b)

$$\frac{v_O}{v_I} = -\frac{R_2}{R_1} \quad (2.9)$$


Finite Open Loop Gain

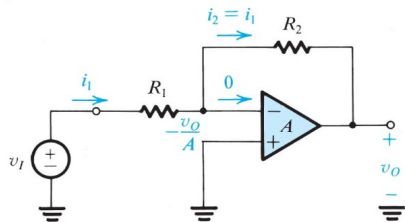


$$\frac{v_O}{v_I} = -\frac{R_2}{R_1} * \frac{1}{1 + (1 + R_2/R_1)/A} \quad (2.5)$$

For negligible *gain error*: $1 + R_2/R_1 \ll A$ (page 104)

A Transresistance Amplifier

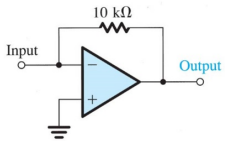


(a)

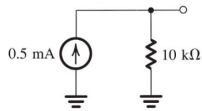


(b)

Basic Non-Inverting Amplifier

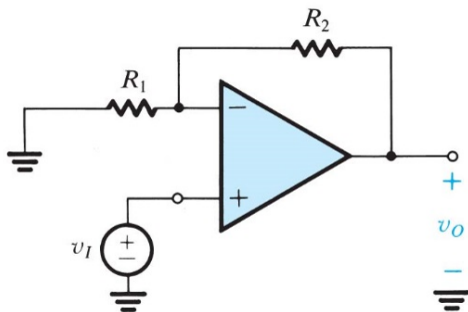

$$\frac{v_O}{v_I} = 1 + \frac{R_2}{R_1} \quad (2.9)$$

Analysis

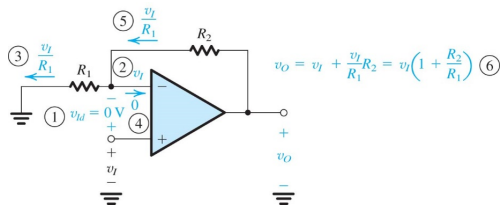


Finite open loop gain


$$\frac{v_O}{v_I} = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + (1 + R_2/R_1)/A} \quad (2.11)$$

For negligible *gain error*: $1 + R_2/R_1 \ll A$ (page 111)

Special Case: The Follower

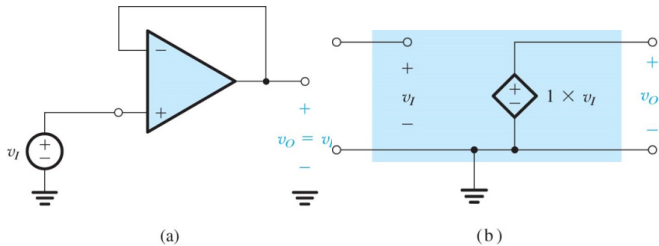


Single OpAmp Differential Amplifier

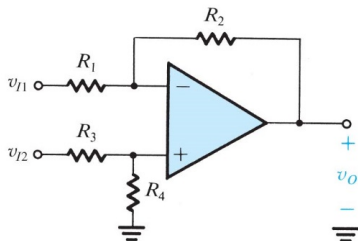


$$\frac{R_4}{R_3} = \frac{R_2}{R_1} = A_D ; (2.15, 2.17)$$

e.g. (and typically) $R_1 = R_3$ and $R_2 = R_4$

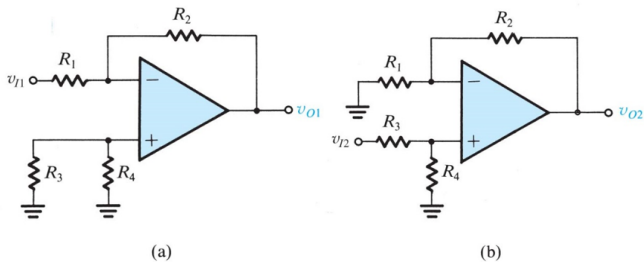Analysing Behaviour With One Input Constant




Common Mode Gain

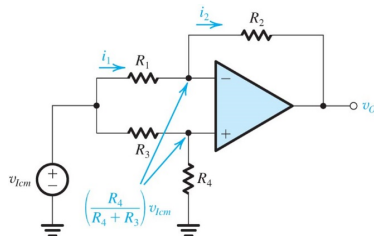

$$A_{cm} \equiv \frac{v_O}{v_{cm}} = \left(\frac{R_4}{R_4 + R_3}\right) \left(1 - \frac{R_2 R_3}{R_1 R_4}\right)$$


ATTENTION: impaired by resistor deviation from nominal value!

Differential Input Resistance

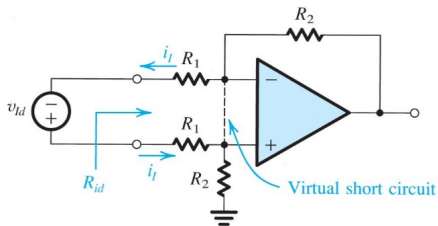


Describing the I/V characteristics (i.e. the load seen) for a differential input source.

Instrumentation amplifier

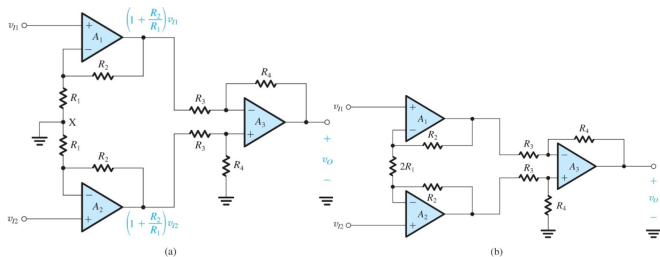


$$A_d \equiv \frac{v_O}{v_{Id}} = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1} \right)$$

Implementing a Variable Gain

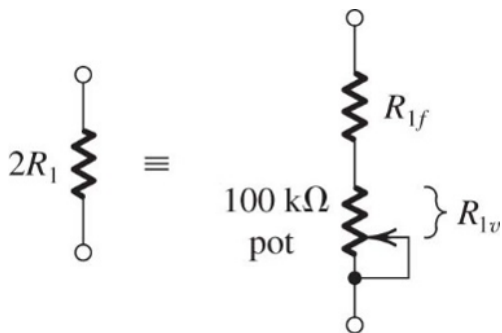

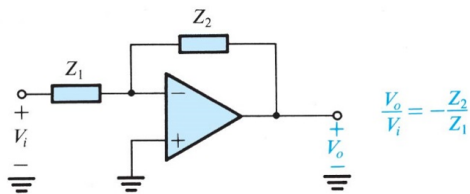
Inverting Amplifier with General Impedances



$$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1}$$

$$\frac{V_O(s)}{V_I(s)} = -\frac{Z_2(s)}{Z_1(s)}$$

Low Pass Amplifier

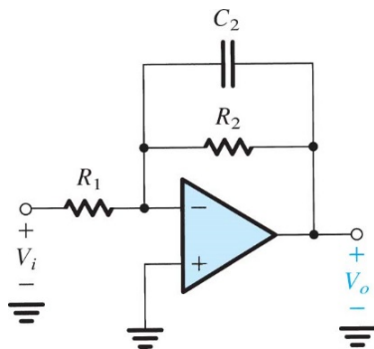

$$\frac{V_O(s)}{V_I(s)} = -\frac{1}{\frac{R_1}{R_2} + sC_2R_1} = -R_2/R_1 \frac{1}{1 + sC_2R_2} \quad (\text{page 125})$$

Content

The Ideal Opamp (book: 2.1)


Some Circuits with OpAmps (book:2.2-2.5)

DC Imperfections (book:2.6)


Closed Loop Frequency Response (book:2.7)

Large Signal (Non-Linear) Effects (book:2.8)


Input Offset Voltage

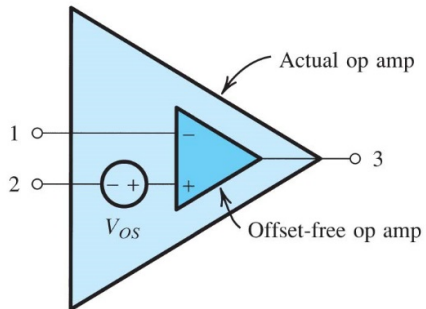


Input Offset Effect

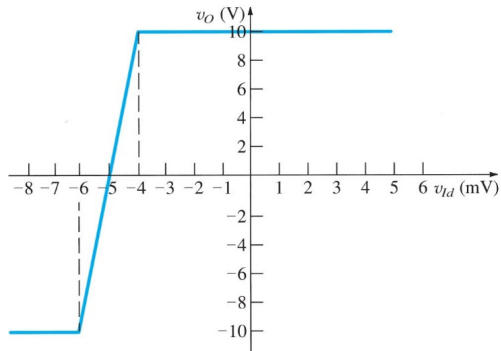

Effect In Closed Loop Negative Amplifier

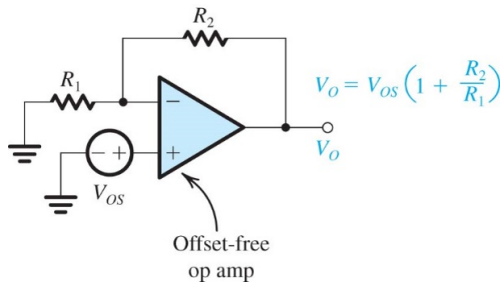

Offset Counter Measure: *AC Coupling*

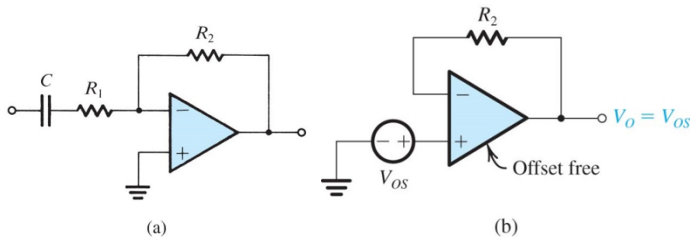

Content

The Ideal Opamp (book: 2.1)

Some Circuits with OpAmps (book:2.2-2.5)

DC Imperfections (book:2.6)

Closed Loop Frequency Response (book:2.7)

Large Signal (Non-Linear) Effects (book:2.8)

General Concept

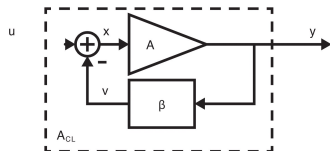


Figure 5.1
© John Wiley & Sons, Inc. All rights reserved.

$$A_{CL} = \frac{y}{u} = \frac{A}{1 + A\beta} = \frac{A}{1 + L}$$

where $L := A\beta$

$$A_{CL} \approx \frac{1}{\beta} \quad \text{for large } L$$

β in inverting and non-inverting amp

non-inverting:

$$\beta = \frac{R_1}{R_1 + R_2}, \quad \frac{1}{\beta} = 1 + \frac{R_2}{R_1}$$

inverting:

$$\beta = \frac{R_1}{R_1 + R_2} / \frac{R_2}{R_1 + R_2}, \quad \frac{1}{\beta} = \frac{R_2}{R_1}$$

Closed Loop Bandwidth Illustration


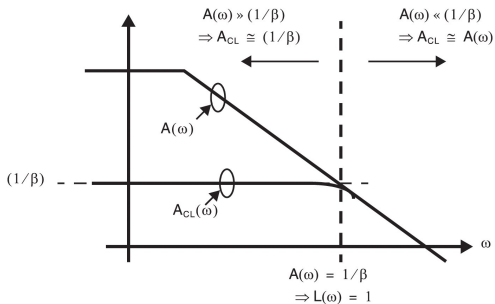


Figure 5.2
© John Wiley & Sons, Inc. All rights reserved.


Provided the feedback loop is purely resistive, i.e. no time constant in the feedback loop.

Example Open Loop Gain

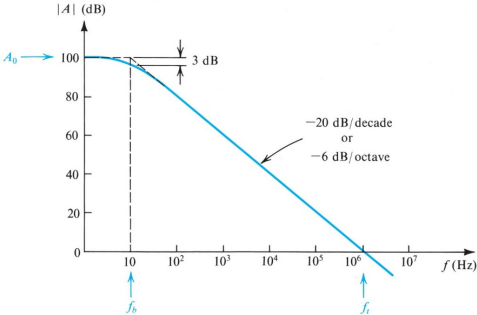

Non-Inverting Example
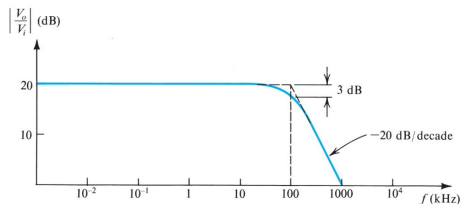
$$R_2/R_1 = 9, \beta = 1/10 \Rightarrow \omega_{3dB} = \frac{\omega_t}{\beta} = 100\text{kHz}$$




Inverting Example

$$R_2/R_1 = 10, \beta = 1/10 \Rightarrow \omega_{3\text{dB}} = \frac{\omega_t}{\beta} = 100\text{kHz}$$

However, the open loop gain with respect to v_I :
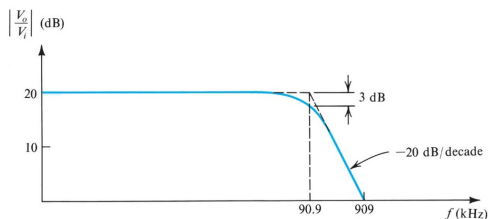
$$\omega'_t = \omega_t \left(\frac{1}{1 + R_1/R_2} \right)$$



Wait for chapter 10 for an explanation!

Content

The Ideal Opamp (book: 2.1)


Some Circuits with OpAmps (book:2.2-2.5)

DC Imperfections (book:2.6)


Closed Loop Frequency Response (book:2.7)

Large Signal (Non-Linear) Effects (book:2.8)


Power Rail Clipping

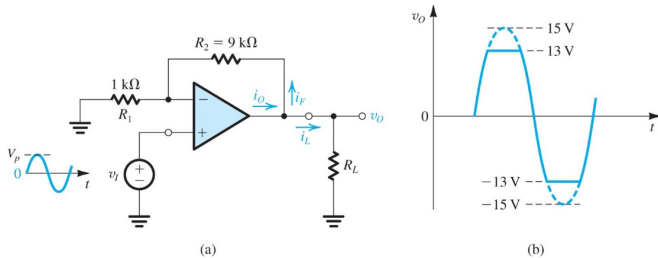


Slew Rate Effect On Step

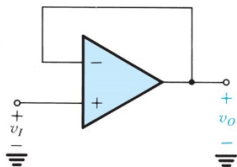


(a)

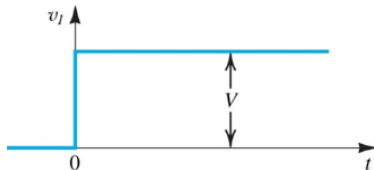

(b)

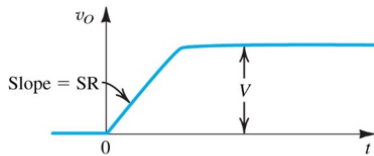

(c)

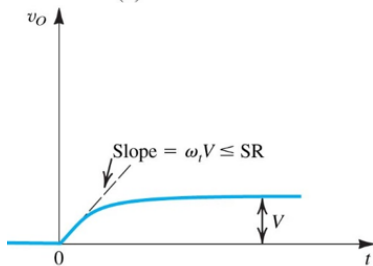

(d)

(similar effect by absolute output current limit)

Slew Rate Effect On Sine

