

# INF4420

## Reference circuits

Spring 2012

Jørgen Andreas Michaelsen (jorgenam@ifi.uio.no)

1 / 47

## Outline

Reference circuits and bias circuits

Uses of reference circuits and bias circuits

MOSFET based references

Parasitic diode based references (bandgaps)

2 / 47

# Reference circuits

"Bandgaps". Why?

Every analog and mixed-signal system needs a stable reference.

The reference circuit presents some physical quantity (voltage, current, frequency, other?)




Image courtesy of Texas Instruments

3 / 47
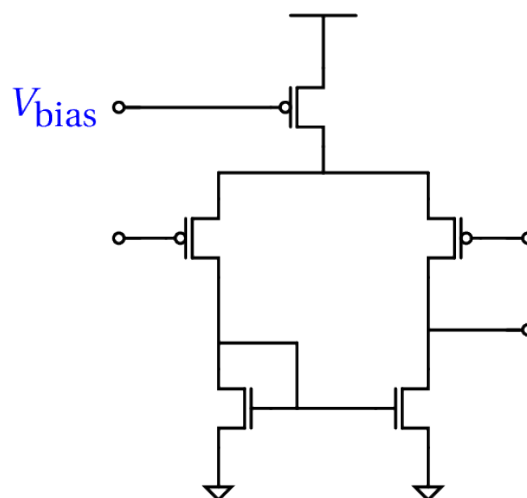
# Biassing an analog circuit

Analog circuits need a current source to set the operating point.

Circuit performance very dependent on the biasing.




4 / 47
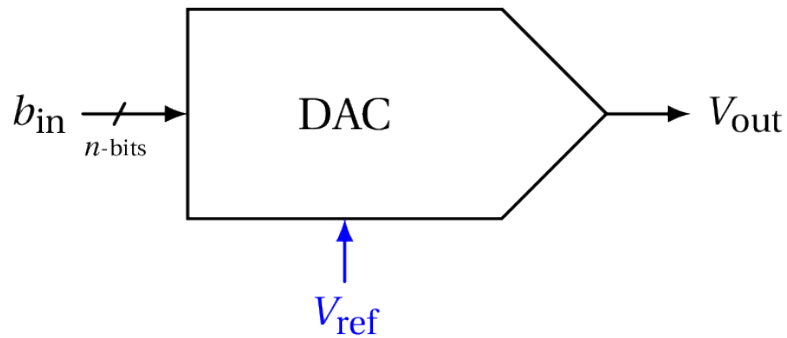
# Data converters


Binary word input is dimensionless.

Need to multiply the dimensionless input with a dimensioned (physical) reference.



5 / 47

# Voltage supply regulation

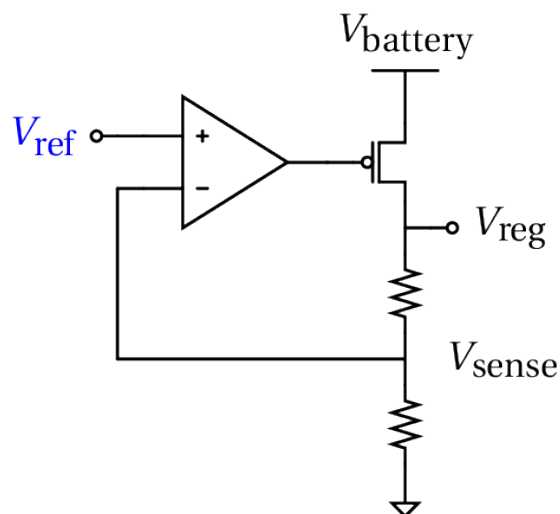

6 / 47

# Temperature behaviour

Predictable behaviour across temperature

- Constant
- Proportional (PTAT)


Additionally, insensitive to supply voltage and process variations (PVT).

7 / 47
 
# A very simple reference

Careful layout gives good matching between resistors

- Temperature affects resistors equally, good TC
- Precisely defined  $V_{ref}$  as ratio of  $V_{dd}$
- Precise value of  $V_{dd}$  is not known (bad)
- Poor PSRR! (bad)




8 / 47

# MOSFET-R reference


Can be used to generate a bias voltage or reference voltage.

Better PSRR than the voltage divider.

 

9 / 47

# MOSFET-R reference

 


10 / 47

# MOSFET-R reference

$$\Rightarrow V_{\text{ref}} = V_{\text{tn}} + \sqrt{\frac{2I_1}{\beta_1}}$$

$$= V_{\text{tn}} + \sqrt{\frac{2(V_{\text{dd}} - V_{\text{ref}})}{R\beta_1}}$$
 
$$\Rightarrow V_{\text{ref}} = V_{\text{tn}} + \frac{\sqrt{1 + 2R\beta_1(V_{\text{dd}} - V_{\text{tn}})} - 1}{R\beta_1}$$




11 / 47

# Beta multiplier reference

Deriving  $I_{\text{ref}}$  from  $I_{\text{out}}$   
Less dependence on  $V_{\text{dd}}$

Can be used for biasing  
and reference

 

12 / 47

## Beta multiplier reference

$$V_{GS1} = V_{GS2} + I_{REF}R$$

$$\sqrt{\frac{2I_{REF}}{\beta_1}} + V_{TN} = \sqrt{\frac{2I_{REF}}{\beta_2}} + V_{TN} + I_{REF}R$$

$$I_{REF} = \frac{2}{\beta_1} \frac{1}{R^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

13 / 47

## Beta multiplier reference

$$I_{REF} = I_{D1} = \frac{2}{\beta_1} \frac{1}{R^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

$$g_{m1} = \sqrt{2\beta_1 I_{D1}} = \frac{2}{R} \left(1 - \frac{1}{\sqrt{K}}\right)$$

$$K = 4 \Rightarrow g_{m1} = \frac{1}{R}$$

14 / 47

## Beta multiplier reference

As a voltage reference, take  $V_{gs1}$  to be the reference voltage,  $V_{ref}$ .

We know the current,  $I_{ref}$ . Use this to find  $V_{gs1}=V_{ref}$

We must find the sensitivity of  $V_{ref}$  to  $V_{dd}$  and  $T$

15 / 47

## Beta multiplier reference

$$I_{REF} = I_{D1} = \frac{2}{\beta_1} \frac{1}{R^2} \left( 1 - \frac{1}{\sqrt{K}} \right)^2$$

$$V_{REF} = V_{GS1} = \sqrt{\frac{2I_{D1}}{\beta_1}} + V_{TN}$$

$$\begin{aligned} \Rightarrow V_{REF} &= \frac{2}{R\beta_1} \left( 1 - \frac{1}{\sqrt{K}} \right) + V_{TN} \\ &= \frac{1}{R\beta_1} + V_{TN}, \text{ with } K = 4 \end{aligned}$$

16 / 47




# Bandgaps

It turns out, we can make references with less temperature dependence using bipolar transistors.

17 / 47

# Temperature independence

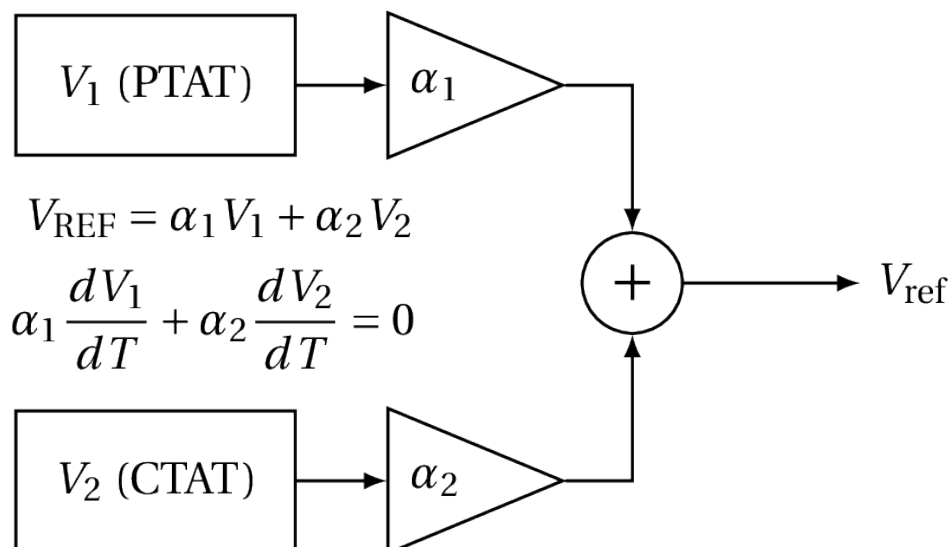

18 / 47

# Parasitic diode CTAT and PTAT

Need elements with well defined temperature behaviour. We will use diode connected BJTs.

CTAT from  $V_{be}$  (biased with constant current)


PTAT from "delta  $V_{be}$ " (biased with ratioed current or emitter area), result is the thermal voltage,  $V_T$

19 / 47
 
# Bipolar transistor diodes

Current sinked by the device is affected by temperature

- $V_T$  is the thermal voltage (proportional to  $T$ ), 26 mV @ RT
- $I_S$  is also a function of temperature



$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

$$V_T = \frac{kT}{q}$$

20 / 47

# PTAT voltage


$$V_{BE} = V_T \ln \frac{I_C}{I_S}$$

$$\Delta V_{BE} = V_{BE1} - V_{BE2}$$

$$= V_T \ln \frac{I_1}{I_S} - V_T \ln \frac{I_1}{nI_S}$$

$$= V_T (\ln I_1 - \ln I_S - \ln I_1 + (\ln n + \ln I_S))$$

$$= V_T \ln n$$

 

21 / 47

# PTAT voltage

To find temperature behaviour, we take the derivative wrt. temperature (assume the first derivative is constant)

Delta Vbe is proportional to absolute temperature.

$$\Delta V_{BE} = V_T \ln n$$


$$V_T = \frac{kT}{q}$$

Defined by two physical constants and emitter ratio, n.

$$\frac{d\Delta V_{BE}}{dT} = \frac{k}{q} \ln n = 86.2 \ln n \frac{\mu V}{K}$$

22 / 47

# PTAT voltage

 

23 / 47

# CTAT voltage

For the full bandgap circuit, we need both PTAT and CTAT.

$I_s$  exhibits temperature dependence. In the  $\Delta V_{BE}$ ,  $I_s$  is canceled. By looking at a single junction  $V_{BE}$ , we get a contribution from  $I_s$ .  $dV_{BE}/dT$  assuming constant current  $I_C$ .

In this case, the overall TC is CTAT.

24 / 47

# CTAT voltage

$$V_{BE} = V_T \ln \frac{I_C}{I_S}$$

$$\frac{dV_{BE}}{dT} = \frac{V_{BE} - (4 + m)V_T - \frac{E_g}{q}}{T}$$

$$(uv)' = u'v' + uv'$$

$$\left(\frac{u}{v}\right)' = \frac{u'v - uv'}{v^2}$$

$$(\ln h(x))' = \frac{h'(x)}{h(x)}$$


$$(x^n)' = nx^{n-1}$$

$$e^u = e^u u'$$

25 / 47

 
# CTAT voltage

Silicon bandgap energy as a function of temperature



26 / 47

# CTAT voltage

 

27 / 47


# Bandgap circuits

We know how to generate PTAT and CTAT, and how we should combine these contributions for temperature independence (i. e. scale and add to achieve temperature independence).

How do we make a circuit that realizes this system?

28 / 47

# Bandgap circuits

 


29 / 47

# Bandgap circuits

Need a circuit that can sense  $V_1$  and  $V_2$  and adjust the current sources so that  $V_1 = V_2$


$$V_2 = V_{be2} + V_t \ln n$$

 $\ln n$  must be 17.2 for  $V_2$  to be independent of  $T$



30 / 47

# Bandgap circuits

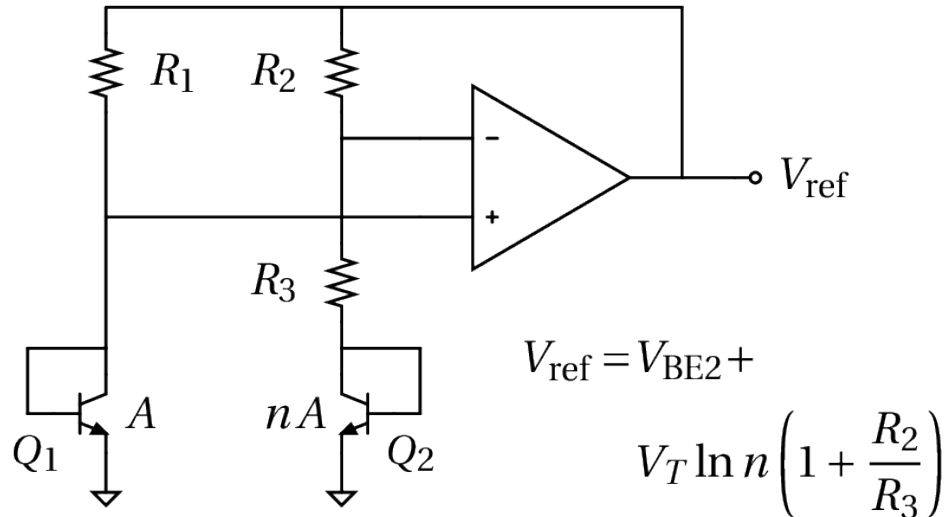

31 / 47

# Bandgap circuits

$$V_{\text{ref}} = V_{\text{BE}2} + V_T \ln n \left( 1 + \frac{R_2}{R_3} \right)$$

$$V_{\text{ref}} = \alpha_1 V_1 + \alpha_2 V_2$$

$$\text{Zero TC} \Rightarrow \alpha_1 \frac{dV_1}{dT} + \alpha_2 \frac{dV_2}{dT} = 0$$

$$\alpha_1 \frac{dV_{\text{BE}2}}{dT} + \alpha_2 \frac{dV_T}{dT} = 0$$

$$\Rightarrow \alpha_1 = 1, \alpha_2 = -\frac{dV_{\text{BE}2}}{dT} \frac{T}{V_T}, \alpha_2 = \ln n \left( 1 + \frac{R_2}{R_3} \right)$$

32 / 47




# Bandgap circuits

This circuit is used for illustration purposes. Working with CMOS, there are a number of issues with this circuit which we will discuss in the following slides. We will try to find circuits which are more practical and CMOS compatible.

33 / 47

 
# A more CMOS friendly BJT

Instead of the diode connected npn that we have used so far, we will use a pnp. This is so that we can implement the device in a CMOS process without any special processing.




34 / 47

# BJT in a CMOS process

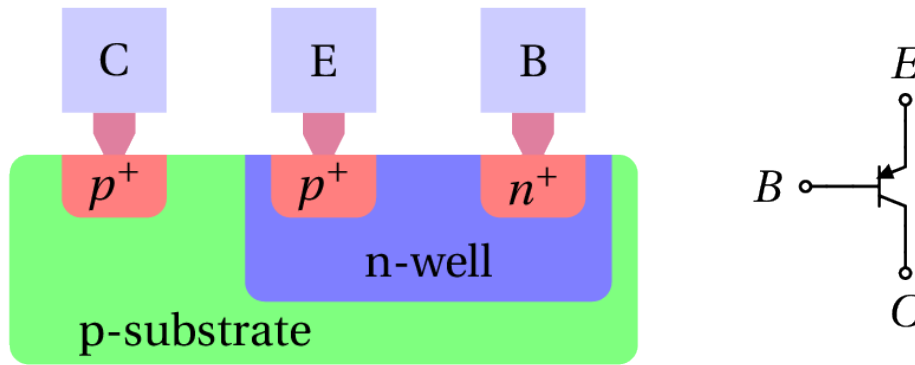


35 / 47

# CMOS bandgap

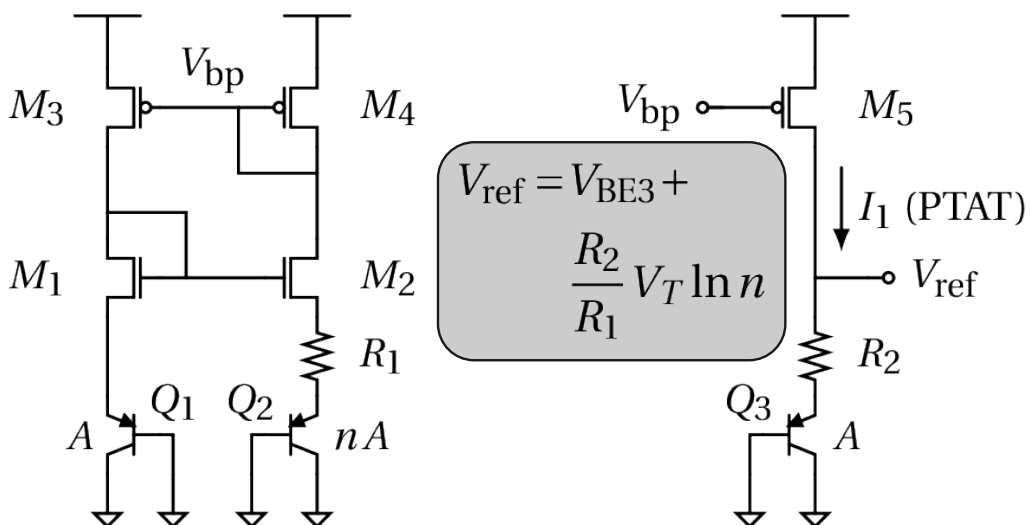


36 / 47

# CMOS bandgap

 

37 / 47

# Low-voltage bandgap

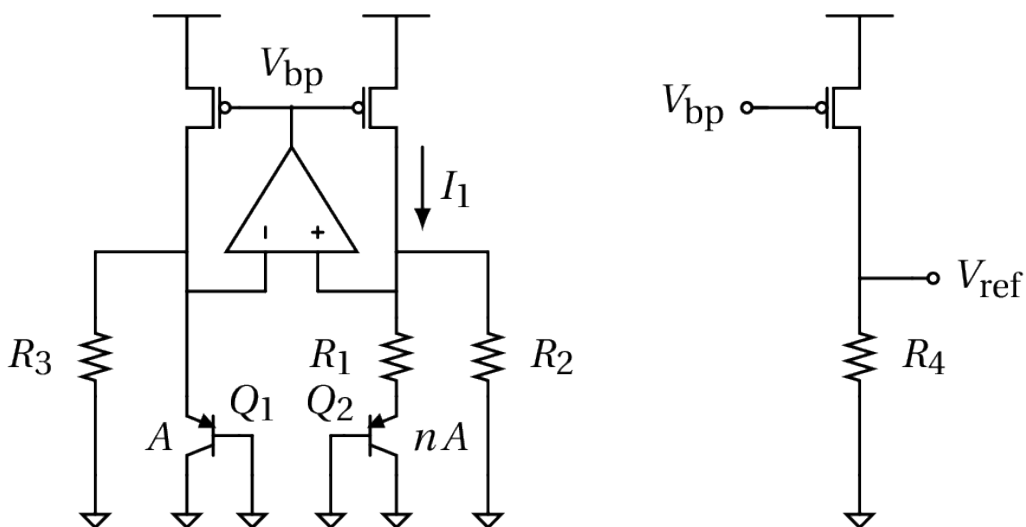

38 / 47

## Low-voltage bandgap


The core circuit is (again) the PTAT current generator. Although the delta  $V_{be}$  gives rise to a PTAT voltage (dropped across  $R_1$ ), the absolute  $V_{be}$  of  $Q_1$  and  $Q_2$  is CTAT.  $V_{be1}$  controls the current through  $R_2$  and  $R_3$ . The result is a temperature independent current if the currents are scaled correctly.

39 / 47

## Low-voltage bandgap

$$\begin{aligned}I_1 &= I_{PTAT} + I_{CTAT} \\I_{PTAT} &= \frac{V_T \ln n}{R_1} \\I_{CTAT} &= \frac{V_{BE1}}{R_3} \\V_{REF} &= R_4 I_1 \\&= \frac{R_4}{R_1} V_T \ln n + \frac{R_4}{R_3} V_{BE1}\end{aligned}$$

40 / 47

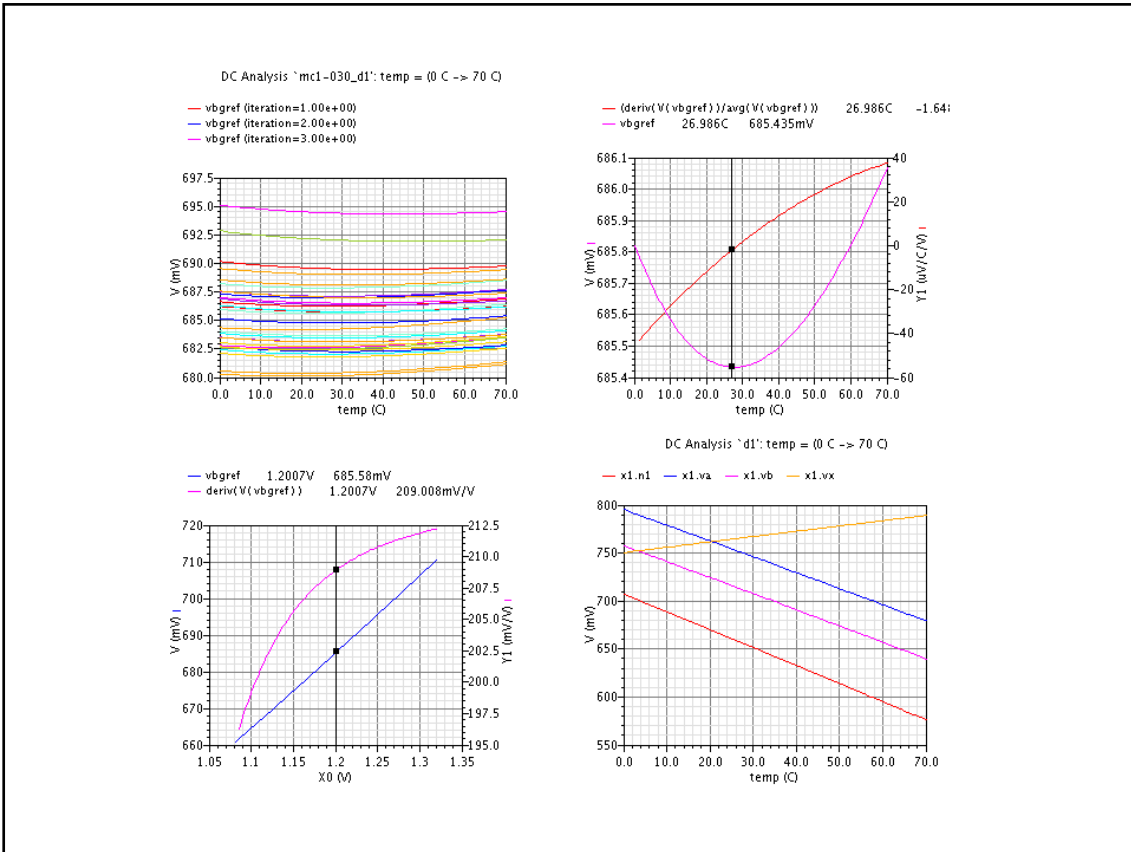

41 / 47

# Stability

Stability is a concern for any system with feedback.

Must make sure that we have more negative feedback than positive.

42 / 47

# Transient response

Transients may capacitively couple to circuit nodes.

Faster opamp

Decoupling (opamp stability)

43 / 47

# Startup circuit

In the discussion so far, we have assumed the circuits are at the desirable operating point.

We must add circuitry to make sure the circuit is not stuck at a "zero" operating point.

Typically a circuit to inject some current if we are at or close to the undesirable operating point. (Power on reset.)

This is very important. Simulator does not necessarily reveal this problem.

44 / 47

# Curvature correction

In our analysis we have assumed the PTAT and CTAT to be constant. This assumption will lead to a non-linearity of the TC (curvature), approximately parabolic shape.

Possible to design some function to try to mitigate this effect.

Even possible to use  $V_{os}$  constructively (Cabrini, ESSCIRC 2005). Not curriculum.

45 / 47

# Bandgap circuit issues


- Collector current variation
- CMOS compatibility (BJTs)
- Opamp offset voltage
- Opamp resistive loading
- Stability
- Startup
- Transient response
- PSRR
- Curvature
- Limited supply voltage
- Noise
- Resistor TC

46 / 47
 
# Online resources

This is not part of the curriculum

<http://www.archive.org/details/APaulBro1989>



A Paul Brokaw